

HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY – VNU HCMC
OFFICE FOR INTERNATIONAL STUDY PROGRAM
FACULTY OF ELECTRICAL AND ELECTRONIC ENGINEERING

————— * —————



DIGITAL SYSTEMS (LAB) EXPERIMENTAL REPORT (Lab 1)

Lecturer : **Mr. Nguyễn Tuấn Hùng**
Subject : **Digital Systems**
Class : **TT06**
Name : **Lương Triển Thắng**
Student ID : **2051194**

Ho Chi Minh City, 31st May, 2022


Contents

I	Laboratory 1:	
	<i>Get started with FPGA</i>	2
1.	Know how to program n -bit wide 2-to-1 multiplexer	2
a.	Code	2
b.	Waveform	3
c.	Result of RTL viewer	3
2.	Known how to program n -bit wide 4-to-1 multiplexer	4
a.	Code	4
b.	Waveform	5
c.	Result of RTL viewer	5
3.	Known how to interface with 7-segment LED	6
a.	Method 1: with MUX	6
b.	Method 2: without MUX	10
c.	Waveform	12
4.	Known how to interface 7-segment LED and multiplexer	13
a.	Code	13
b.	Waveform	16
c.	Result of RTL viewer	17
5.	Known how to interface 7-segment LED and multiplexer	19
a.	Method 1: with MUX, comparator and “Circuit A”	19
b.	Method 2: using conditions in VHDL	24
c.	Waveform	26

I Laboratory 1

Get started with FPGA

 1. Know how to program n -bit wide 2-to-1 multiplexer



Circuit diagram

a. Code

MUX.vhdl

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY MUX IS
    PORT (
        a : IN std_logic;
        sel : IN std_logic;
        b : IN std_logic;
        z : OUT std_logic
    );
END ENTITY;

ARCHITECTURE arch OF MUX IS
BEGIN
    z <= (NOT(sel) AND a) OR (sel AND b);
END arch;
```

Exc1.vhdl

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Exc1 IS
    PORT (
        x : IN std_logic_vector(3 DOWNTO 0);
        y : IN std_logic_vector(3 DOWNTO 0);
        s : IN std_logic;
        sOUT : OUT std_logic;
        m : OUT std_logic_vector(3 DOWNTO 0)
    );
END ENTITY;

ARCHITECTURE behave OF Exc1 IS
    COMPONENT MUX IS
        PORT (
            a : IN std_logic;
```

```

        sel : IN std_logic;
        b : IN std_logic;
        z : OUT std_logic

    );
END COMPONENT;


BEGIN

sOUT <= s;
gen : FOR i IN 3 DOWNTO 0 GENERATE
    MUX4 : MUX
    PORT MAP(
        a => x(i),
        b => y(i),
        sel => s,
        z => m(i)
    );
END GENERATE;


END ARCHITECTURE;

```


b. Waveform

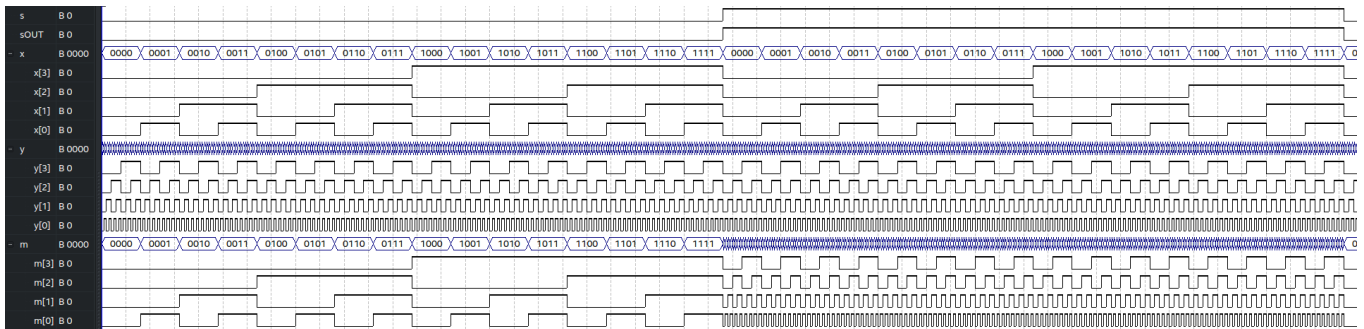

c. Result of RTL viewer

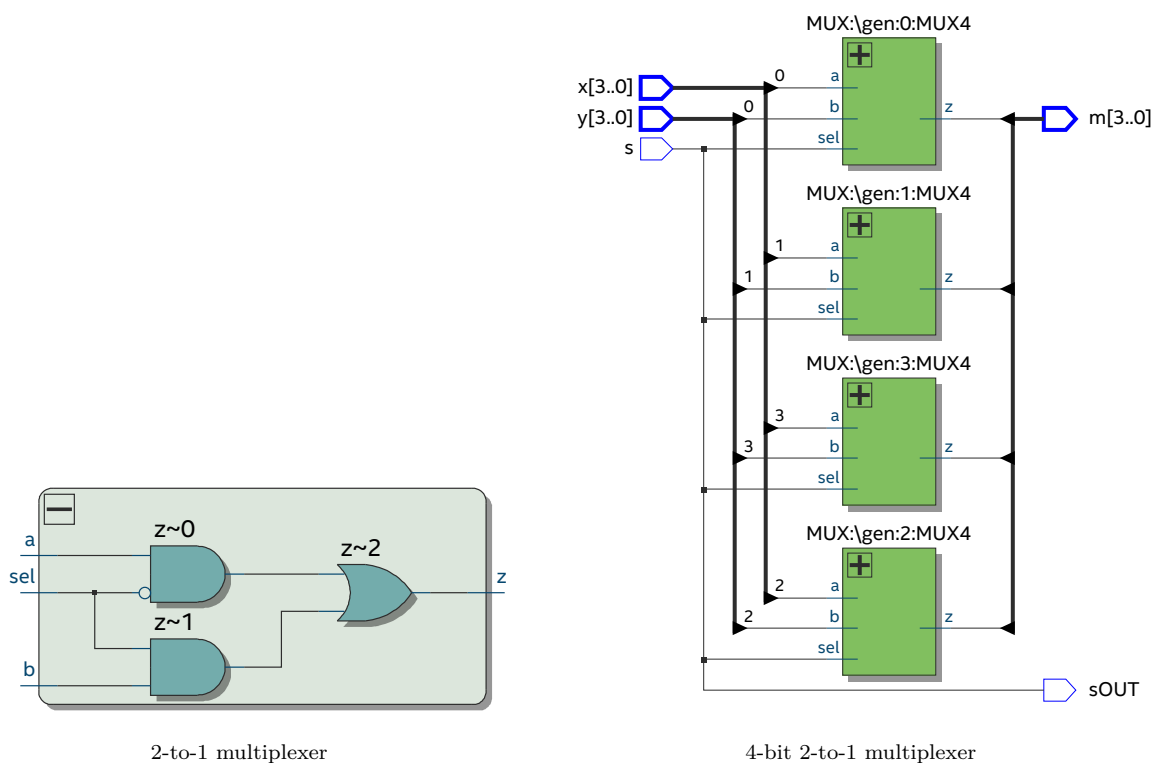

 2. Known how to program n-bit wide 4-to-1 multiplexer



Circuit diagram

a. Code

Four2OneMUX.vhdl

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Four2OneMUX IS
    PORT (
        s : IN std_logic_vector(1 DOWNTO 0);
        u : IN std_logic;
        v : IN std_logic;
        w : IN std_logic;
        x : IN std_logic;
        m : OUT std_logic
    );
END ENTITY;

ARCHITECTURE behave OF Four2OneMUX IS
BEGIN
    WITH s SELECT
        m <= u WHEN "00",
            v WHEN "01",
            w WHEN "10",
            x WHEN "11";

END ARCHITECTURE;
```

Exc1.vhdl

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Exc2 IS
    PORT (
        ss : IN std_logic_vector(1 DOWNTO 0);
        uu : IN std_logic_vector(1 DOWNTO 0);
        vv : IN std_logic_vector(1 DOWNTO 0);
        ww : IN std_logic_vector(1 DOWNTO 0);
        xx : IN std_logic_vector(1 DOWNTO 0);
        mm : OUT std_logic_vector(1 DOWNTO 0)
    );
END ENTITY;

ARCHITECTURE behave OF Exc2 IS
```


```

COMPONENT Four2OneMUX IS
    PORT (
        s : IN std_logic_vector(1 DOWNTO 0);
        u : IN std_logic;
        v : IN std_logic;
        w : IN std_logic;
        x : IN std_logic;
        m : OUT std_logic
    );
END COMPONENT;


BEGIN
    gen : FOR i IN 1 DOWNTO 0 GENERATE
        MUX2 : Four2OneMUX
            PORT MAP(
                s => ss,
                u => uu(i),
                v => vv(i),
                w => ww(i),
                x => xx(i),
                m => mm(i)
            );
    END GENERATE;
END ARCHITECTURE;

```

b. Waveform

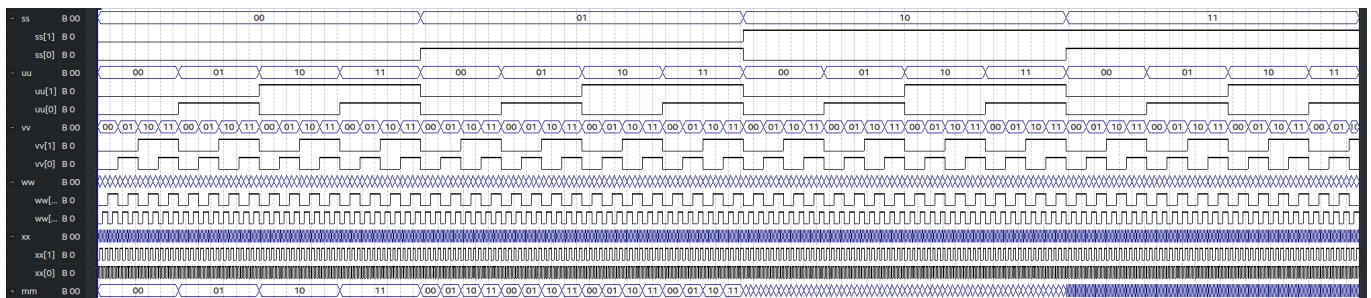

c. Result of RTL viewer

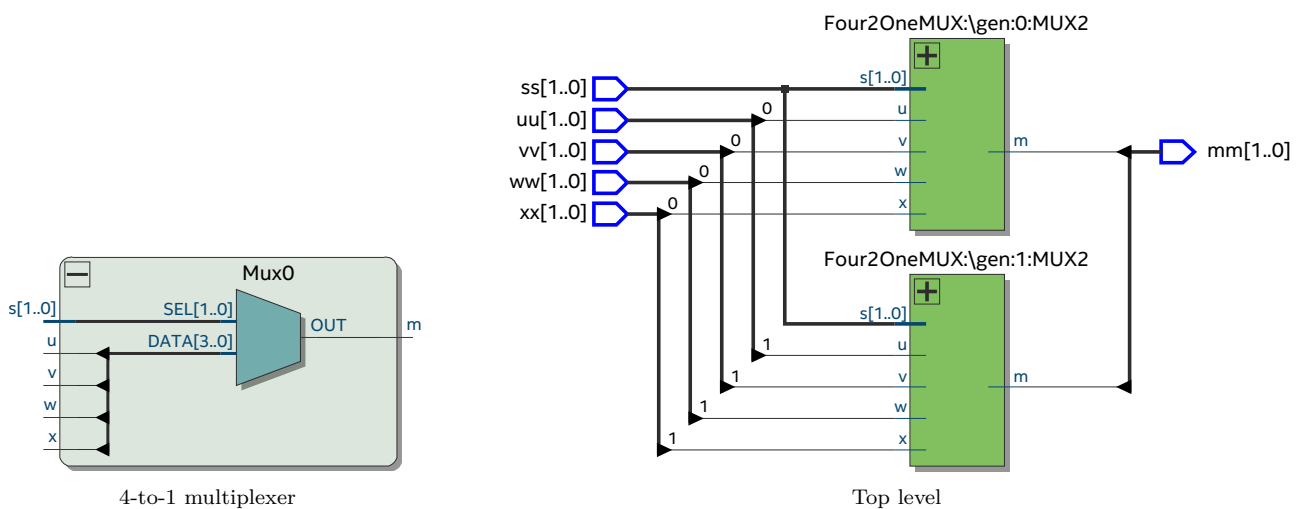

3. Known how to interface with 7-segment LED

s_1	s_0	LEDs			
0	0	8	8	8	0
0	1	8	8	0	8
1	0	8	0	8	8
1	1	0	8	8	8

a. Method 1: with MUX

Code

DE10.vhdl

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY DE10 IS
    PORT (
        c : IN std_logic_vector(1 DOWNTO 0);
        HEXn : OUT std_logic_vector(0 TO 6)
    );
END DE10;

ARCHITECTURE behavior OF DE10 IS
    SIGNAL HEX : std_logic_vector(0 TO 6);
BEGIN
    HEXn <= NOT(HEX);
    WITH c SELECT
    HEX <= "0111101" WHEN "00",
           "1001111" WHEN "01",
           "0110000" WHEN "10",
           "1111110" WHEN "11",
           "0000000" WHEN OTHERS;
END behavior;

```

Four2OneMUX.vhdl

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Four2OneMUX IS
    PORT (
        s : IN std_logic_vector(1 DOWNTO 0);
        u : IN std_logic;
        v : IN std_logic;
        w : IN std_logic;
        x : IN std_logic;
        m : OUT std_logic
    );
END ENTITY;

ARCHITECTURE behave OF Four2OneMUX IS
BEGIN
    WITH s SELECT
    m <= u WHEN "00",

```

```

        v WHEN "01",
        w WHEN "10",
        x WHEN "11";

END ARCHITECTURE;

TwoBitFour2OneMUX.vhdl

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY TwoBitFour2OneMUX IS
    PORT (
        ss : IN std_logic_vector(1 DOWNTO 0);
        uu : IN std_logic_vector(1 DOWNTO 0);
        vv : IN std_logic_vector(1 DOWNTO 0);
        ww : IN std_logic_vector(1 DOWNTO 0);
        xx : IN std_logic_vector(1 DOWNTO 0);
        mm : OUT std_logic_vector(1 DOWNTO 0)
    );
END ENTITY;

ARCHITECTURE behave OF TwoBitFour2OneMUX IS
    COMPONENT Four2OneMUX IS
        PORT (
            s : IN std_logic_vector(1 DOWNTO 0);
            u : IN std_logic;
            v : IN std_logic;
            w : IN std_logic;
            x : IN std_logic;
            m : OUT std_logic
        );
    END COMPONENT;

BEGIN
    gen : FOR i IN 1 DOWNTO 0 GENERATE
        MUX2 : Four2OneMUX
            PORT MAP(
                s => ss,
                u => uu(i),
                v => vv(i),
                w => ww(i),
                x => xx(i),
                m => mm(i)
            );
    END GENERATE;

END ARCHITECTURE;

```

```

Exc1.vhdl

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Exc3 IS
    PORT (
        SW : IN std_logic_vector(9 DOWNTO 0);
        HEX0 : OUT std_logic_vector(0 TO 6);
        HEX1 : OUT std_logic_vector(0 TO 6);
        HEX2 : OUT std_logic_vector(0 TO 6);
        HEX3 : OUT std_logic_vector(0 TO 6)
    );
END ENTITY;

```



```

ARCHITECTURE behave OF Exc3 IS
    SIGNAL sel3, sel2, sel1, sel0, selct : std_logic_vector(1 DOWNTO 0);
    SIGNAL outHEX3, outHEX2, outHEX1, outHEX0 : std_logic_vector(1 DOWNTO 0);

    COMPONENT DE10 IS
        PORT (
            c : IN std_logic_vector(1 DOWNTO 0);
            HEXn : OUT std_logic_vector(0 TO 6)
        );
    END COMPONENT;

    COMPONENT TwoBitFour2OneMUX IS
        PORT (
            ss : IN std_logic_vector(1 DOWNTO 0);
            uu : IN std_logic_vector(1 DOWNTO 0);
            vv : IN std_logic_vector(1 DOWNTO 0);
            ww : IN std_logic_vector(1 DOWNTO 0);
            xx : IN std_logic_vector(1 DOWNTO 0);
            mm : OUT std_logic_vector(1 DOWNTO 0)
        );
    END COMPONENT;


BEGIN
    selct <= SW(9 DOWNTO 8);
    sel3 <= SW(7 DOWNTO 6);
    sel2 <= SW(5 DOWNTO 4);
    sel1 <= SW(3 DOWNTO 2);
    sel0 <= SW(1 DOWNTO 0);
    MUX3 : TwoBitFour2OneMUX
    PORT MAP(
        uu => sel3, vv => sel2, ww => sel1, xx => sel0, ss => selct, mm => outHEX3
    );
    MUX2 : TwoBitFour2OneMUX
    PORT MAP(
        uu => sel2, vv => sel1, ww => sel0, xx => sel3, ss => selct, mm => outHEX2
    );
    MUX1 : TwoBitFour2OneMUX
    PORT MAP(
        uu => sel1, vv => sel0, ww => sel3, xx => sel2, ss => selct, mm => outHEX1
    );
    MUX0 : TwoBitFour2OneMUX
    PORT MAP(
        uu => sel0, vv => sel3, ww => sel2, xx => sel1, ss => selct, mm => outHEX0
    );

    HEX03 : DE10
    PORT MAP(c => outHEX3, HEXn => HEX3);
    HEX02 : DE10
    PORT MAP(c => outHEX2, HEXn => HEX2);
    HEX01 : DE10
    PORT MAP(c => outHEX1, HEXn => HEX1);
    HEX00 : DE10
    PORT MAP(c => outHEX0, HEXn => HEX0);


END ARCHITECTURE;

```


Result of RTL viewer

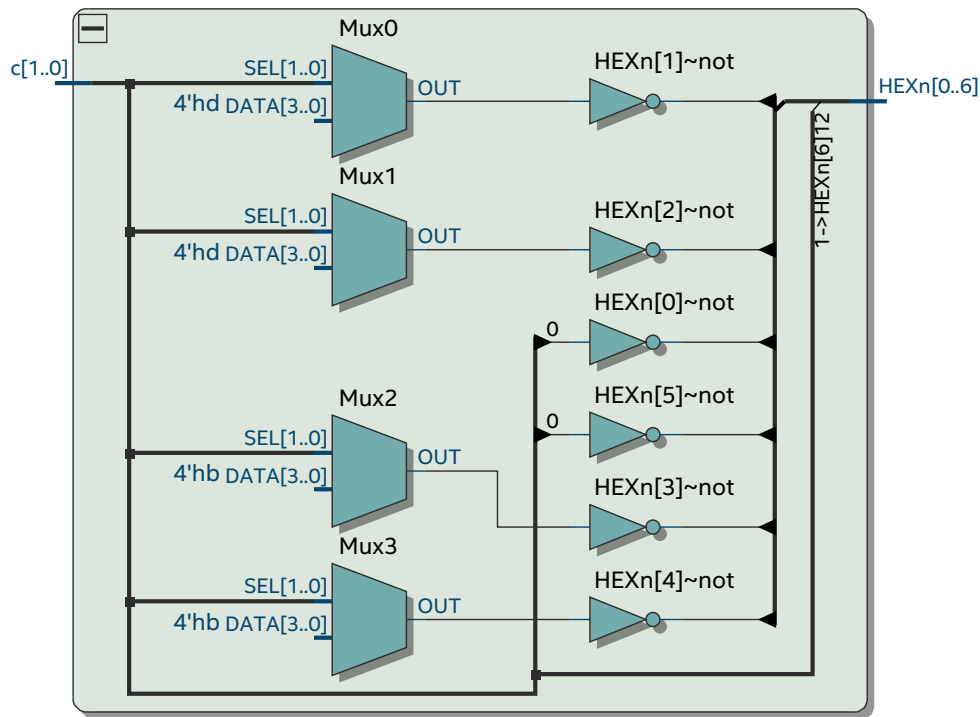


"dE10" 7-segment decoder

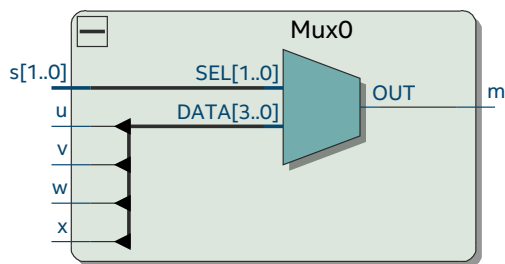

4-to-1 multiplexer

 

2-bit 4-to-1 multiplexer

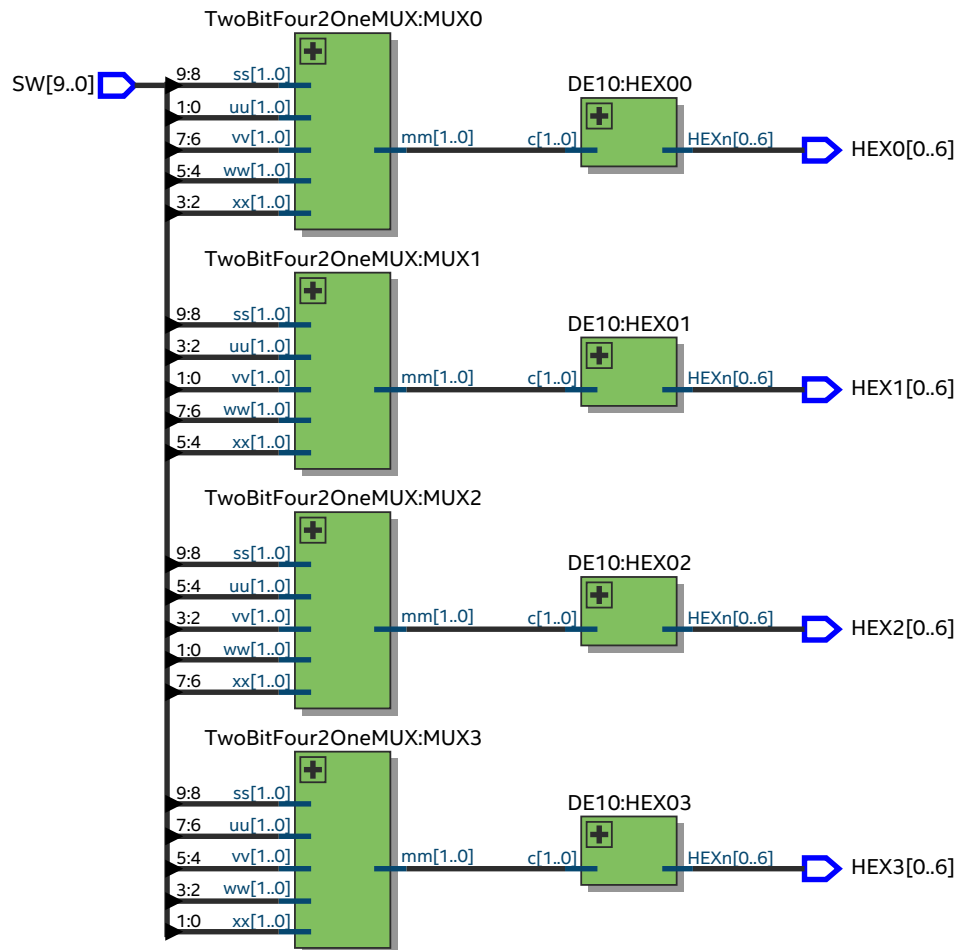

Top level

b. Method 2: without MUX

Code

DE10.vhdl

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY DE10 IS
    PORT (
        c : IN std_logic_vector(1 DOWNTO 0);
        HEXn : OUT std_logic_vector(0 TO 6)
    );
END DE10;

ARCHITECTURE behavior OF DE10 IS
    SIGNAL HEX : std_logic_vector(0 TO 6);
BEGIN
    HEXn <= NOT(HEX);
    WITH c SELECT
    HEX <= "0111101" WHEN "00",
           "1001111" WHEN "01",
           "0110000" WHEN "10",
           "1111110" WHEN "11",
           "0000000" WHEN OTHERS;
END behavior;

```

Exc1.vhdl

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

ENTITY Exc3 IS
    PORT (
        SW : IN std_logic_vector(9 DOWNTO 0);
        HEX0 : OUT std_logic_vector(0 TO 6);
        HEX1 : OUT std_logic_vector(0 TO 6);
        HEX2 : OUT std_logic_vector(0 TO 6);
        HEX3 : OUT std_logic_vector(0 TO 6)
    );
END ENTITY;

ARCHITECTURE behave OF Exc3 IS
    SIGNAL sel3, sel2, sel1, sel0 : std_logic_vector(1 DOWNTO 0);

    COMPONENT DE10 IS
        PORT (
            c : IN std_logic_vector(1 DOWNTO 0);
            HEXn : OUT std_logic_vector(0 TO 6)
        );
    END COMPONENT;


BEGIN
    sel3 <= std_logic_vector(unsigned(SW(7 DOWNTO 6)) + unsigned(SW(9 DOWNTO 8)));
    sel2 <= std_logic_vector(unsigned(SW(5 DOWNTO 4)) + unsigned(SW(9 DOWNTO 8)));
    sel1 <= std_logic_vector(unsigned(SW(3 DOWNTO 2)) + unsigned(SW(9 DOWNTO 8)));
    sel0 <= std_logic_vector(unsigned(SW(1 DOWNTO 0)) + unsigned(SW(9 DOWNTO 8)));

    HEX03 : DE10 PORT MAP(c => sel3, HEXn => HEX3);
    HEX02 : DE10 PORT MAP(c => sel2, HEXn => HEX2);
    HEX01 : DE10 PORT MAP(c => sel1, HEXn => HEX1);
    HEX00 : DE10 PORT MAP(c => sel0, HEXn => HEX0);


END ARCHITECTURE;

```


Result of RTL viewer

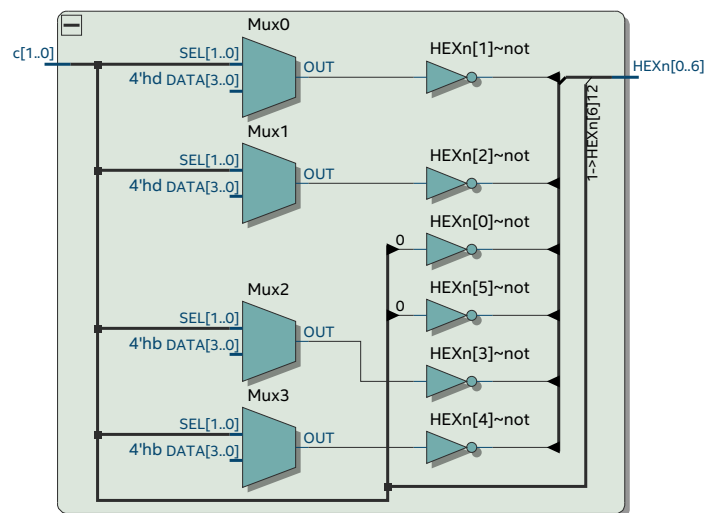

“dE10” 7-segment decoder

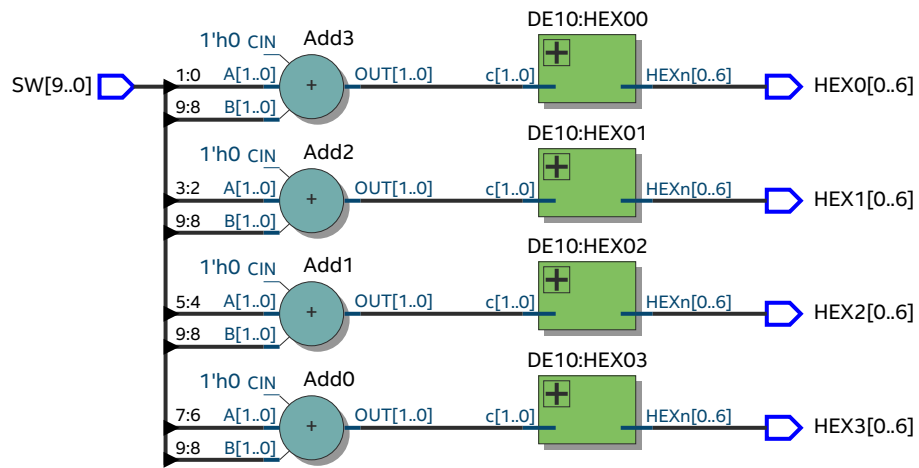

c. Waveform

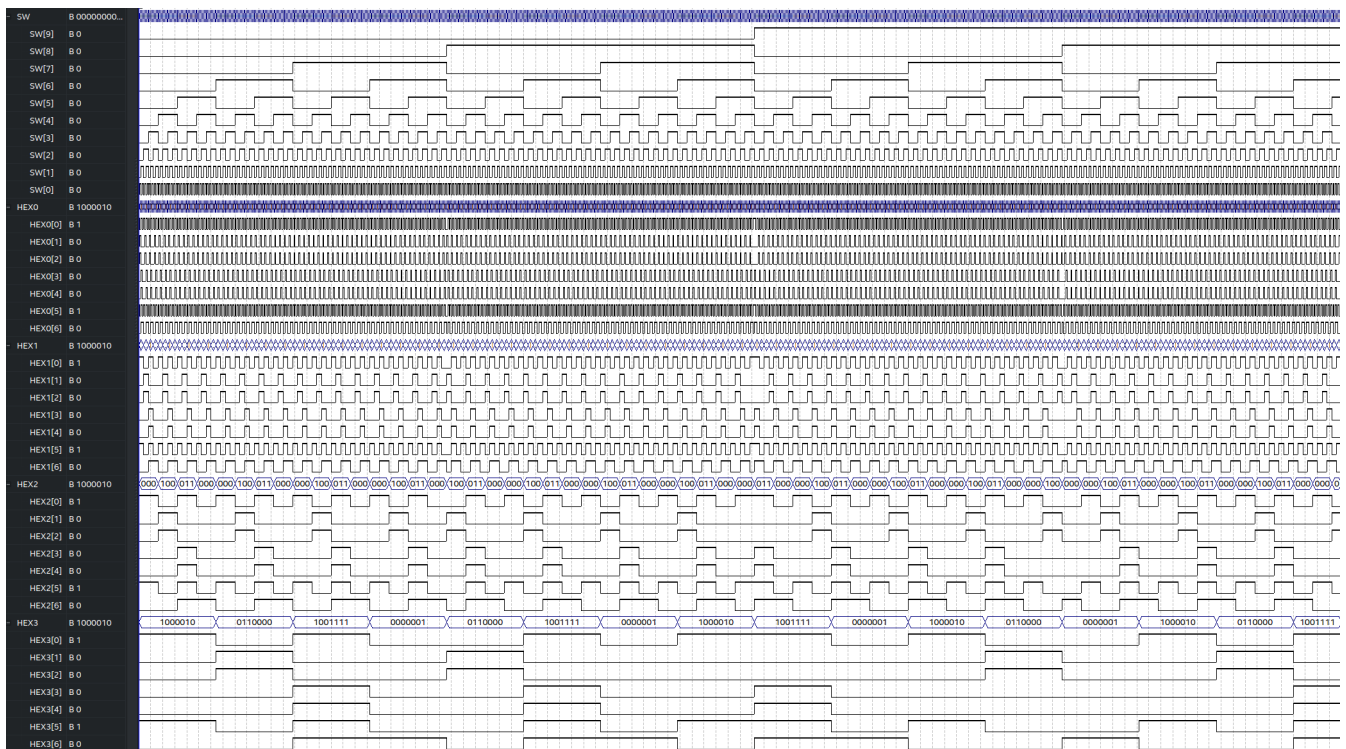

4. Known how to interface 7-segment LED and multiplexer

s_2	s_1	s_0	LEDs					
0	0	0	8	8	0	0	0	0
0	0	1	8	8	8	0	0	0
0	1	0	0	8	8	8	0	0
0	1	1	0	0	8	8	8	0
1	0	0	0	0	0	8	8	8
1	0	1	8	0	0	0	8	8
1	1	0	8	8	8	8	8	8
1	1	1	8	8	8	8	8	8

a. Code

HELLO.vhdl

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY HELLO IS
    PORT (
        c : IN std_logic_vector(2 DOWNTO 0);
        HEXn : OUT std_logic_vector(0 TO 6)
    );
END HELLO;

ARCHITECTURE behavior OF HELLO IS
    SIGNAL HEX : std_logic_vector(0 TO 6);
BEGIN
    HEXn <= NOT(HEX);
    WITH c SELECT
    HEX <= "0110111" WHEN "000",
           "1001111" WHEN "001",
           "0001110" WHEN "010",
           "1111110" WHEN "011",
           "0000000" WHEN OTHERS;
END behavior;

```

Six2OneMUX.vhdl

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Six2OneMUX IS
    PORT (
        s : IN std_logic_vector(2 DOWNTO 0);
        u : IN std_logic;
        v : IN std_logic;
        w : IN std_logic;
        x : IN std_logic;
    );

```

```

        y : IN std_logic;
        z : IN std_logic;
        m : OUT std_logic
    );
END ENTITY;

ARCHITECTURE behave OF Six2OneMUX IS
BEGIN
    WITH s SELECT
    m <= u WHEN "000",
        v WHEN "001",
        w WHEN "010",
        x WHEN "011",
        y WHEN "100",
        z WHEN "101",
        '1' WHEN OTHERS;

END ARCHITECTURE;

```

ThreeBitSix2OneMUX.vhdl

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY ThreeBitSix2OneMUX IS
    PORT (
        ss : IN std_logic_vector(2 DOWNTO 0);
        uu : IN std_logic_vector(2 DOWNTO 0);
        vv : IN std_logic_vector(2 DOWNTO 0);
        ww : IN std_logic_vector(2 DOWNTO 0);
        xx : IN std_logic_vector(2 DOWNTO 0);
        yy : IN std_logic_vector(2 DOWNTO 0);
        zz : IN std_logic_vector(2 DOWNTO 0);
        mm : OUT std_logic_vector(2 DOWNTO 0)
    );
END ENTITY;

ARCHITECTURE behave OF ThreeBitSix2OneMUX IS
    COMPONENT Six2OneMUX IS
        PORT (
            s : IN std_logic_vector(2 DOWNTO 0);
            u : IN std_logic;
            v : IN std_logic;
            w : IN std_logic;
            x : IN std_logic;
            y : IN std_logic;
            z : IN std_logic;
            m : OUT std_logic
        );
    END COMPONENT;

BEGIN
    gen : FOR i IN 2 DOWNTO 0 GENERATE
        MUX2 : Six2OneMUX
        PORT MAP(
            s => ss,
            u => uu(i),
            v => vv(i),
            w => ww(i),
            x => xx(i),
            y => yy(i),
            z => zz(i),
            m => mm(i)
        );
    END GENERATE;
END ARCHITECTURE;

```

```

        );
    END GENERATE;

END ARCHITECTURE;

HELLO.vhdl

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Exc4 IS
    PORT (
        SW : IN std_logic_vector(2 DOWNTO 0);
        HEX0 : OUT std_logic_vector(0 TO 6);
        HEX1 : OUT std_logic_vector(0 TO 6);
        HEX2 : OUT std_logic_vector(0 TO 6);
        HEX3 : OUT std_logic_vector(0 TO 6);
        HEX4 : OUT std_logic_vector(0 TO 6);
        HEX5 : OUT std_logic_vector(0 TO 6)
    );
END ENTITY;

ARCHITECTURE behave OF Exc4 IS
    SIGNAL sel5, sel4, sel3, sel2, sel1, sel0, selct : std_logic_vector(2 DOWNTO 0);
    SIGNAL outHEX5, outHEX4, outHEX3, outHEX2, outHEX1, outHEX0 : std_logic_vector(2 DOWNTO 0);

    COMPONENT HELLO IS
        PORT (
            c : IN std_logic_vector(2 DOWNTO 0);
            HEXn : OUT std_logic_vector(0 TO 6)
        );
    END COMPONENT;

    COMPONENT ThreeBitSix2OneMUX IS
        PORT (
            ss : IN std_logic_vector(2 DOWNTO 0);
            uu : IN std_logic_vector(2 DOWNTO 0);
            vv : IN std_logic_vector(2 DOWNTO 0);
            ww : IN std_logic_vector(2 DOWNTO 0);
            xx : IN std_logic_vector(2 DOWNTO 0);
            yy : IN std_logic_vector(2 DOWNTO 0);
            zz : IN std_logic_vector(2 DOWNTO 0);
            mm : OUT std_logic_vector(2 DOWNTO 0)
        );
    END COMPONENT;

BEGIN
    selct <= SW(2 DOWNTO 0);

    -- HELLO
    sel5 <= "000";
    sel4 <= "001";
    sel3 <= "010";
    sel2 <= "010";
    sel1 <= "011";
    sel0 <= "100";

    MUX5 : ThreeBitSix2OneMUX
    PORT MAP(
        uu => sel5, vv => sel0, ww => sel1, xx => sel2, yy => sel3,
        zz => sel4, ss => selct, mm => outHEX5
    );
    MUX4 : ThreeBitSix2OneMUX

```



```


PORT MAP(
    uu => sel4, vv => sel5, ww => sel0, xx => sel1, yy => sel2,
    zz => sel3, ss => selct, mm => outHEX4
);
MUX3 : ThreeBitSix2OneMUX
PORT MAP(
    uu => sel3, vv => sel4, ww => sel5, xx => sel0, yy => sel1,
    zz => sel2, ss => selct, mm => outHEX3
);
MUX2 : ThreeBitSix2OneMUX
PORT MAP(
    uu => sel2, vv => sel3, ww => sel4, xx => sel5, yy => sel0,
    zz => sel1, ss => selct, mm => outHEX2
);
MUX1 : ThreeBitSix2OneMUX
PORT MAP(
    uu => sel1, vv => sel2, ww => sel3, xx => sel4, yy => sel5,
    zz => sel0, ss => selct, mm => outHEX1
);
MUX0 : ThreeBitSix2OneMUX
PORT MAP(
    uu => sel0, vv => sel1, ww => sel2, xx => sel3, yy => sel4,
    zz => sel5, ss => selct, mm => outHEX0
);

HEX05 : HELLO PORT MAP(c => outHEX5, HEXn => HEX5);
HEX04 : HELLO PORT MAP(c => outHEX4, HEXn => HEX4);
HEX03 : HELLO PORT MAP(c => outHEX3, HEXn => HEX3);
HEX02 : HELLO PORT MAP(c => outHEX2, HEXn => HEX2);
HEX01 : HELLO PORT MAP(c => outHEX1, HEXn => HEX1);
HEX00 : HELLO PORT MAP(c => outHEX0, HEXn => HEX0);


```

END ARCHITECTURE;


b. Waveform

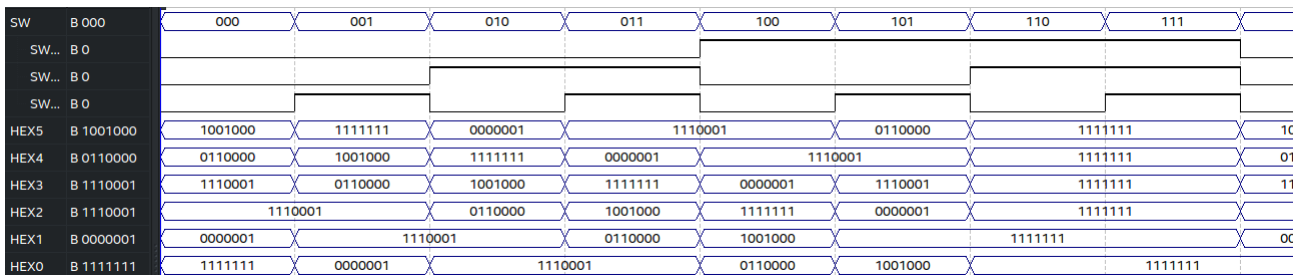


c. Result of RTL viewer

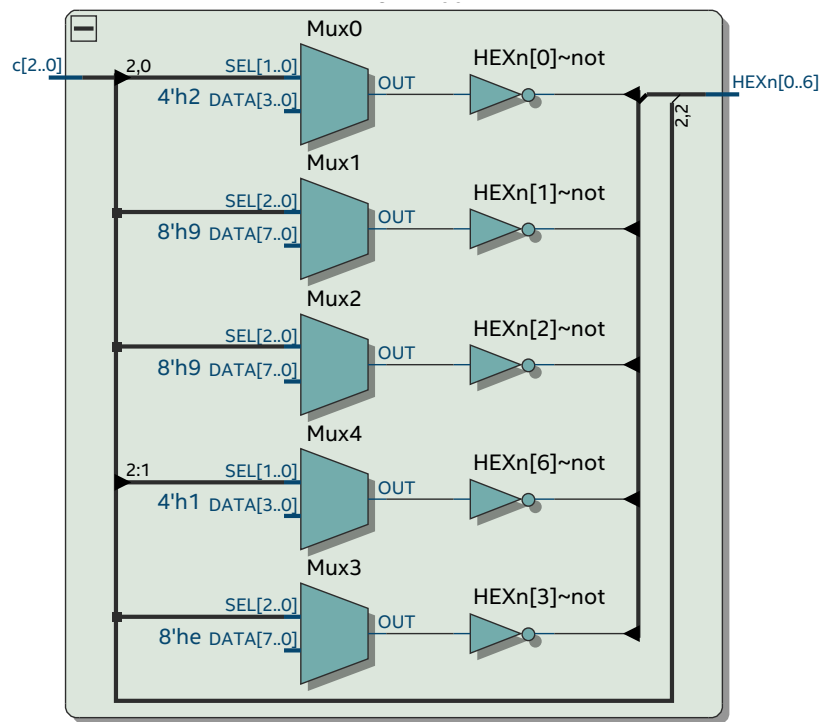


“HELLO” 7-segment decoder

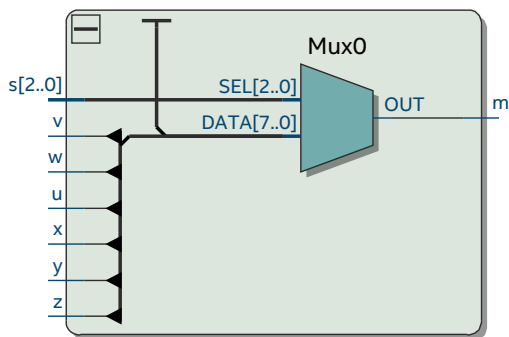

6-to-1 multiplexer

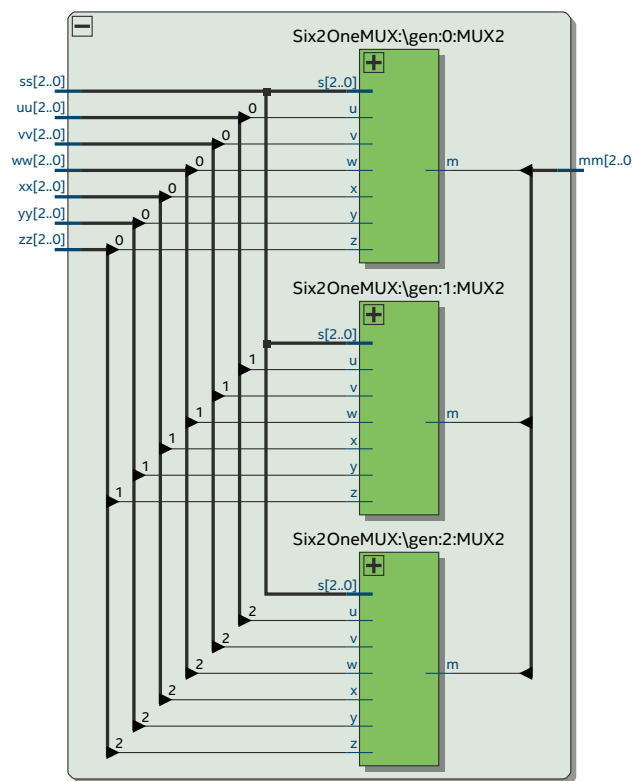

3-bit 6-to-1 multiplexer

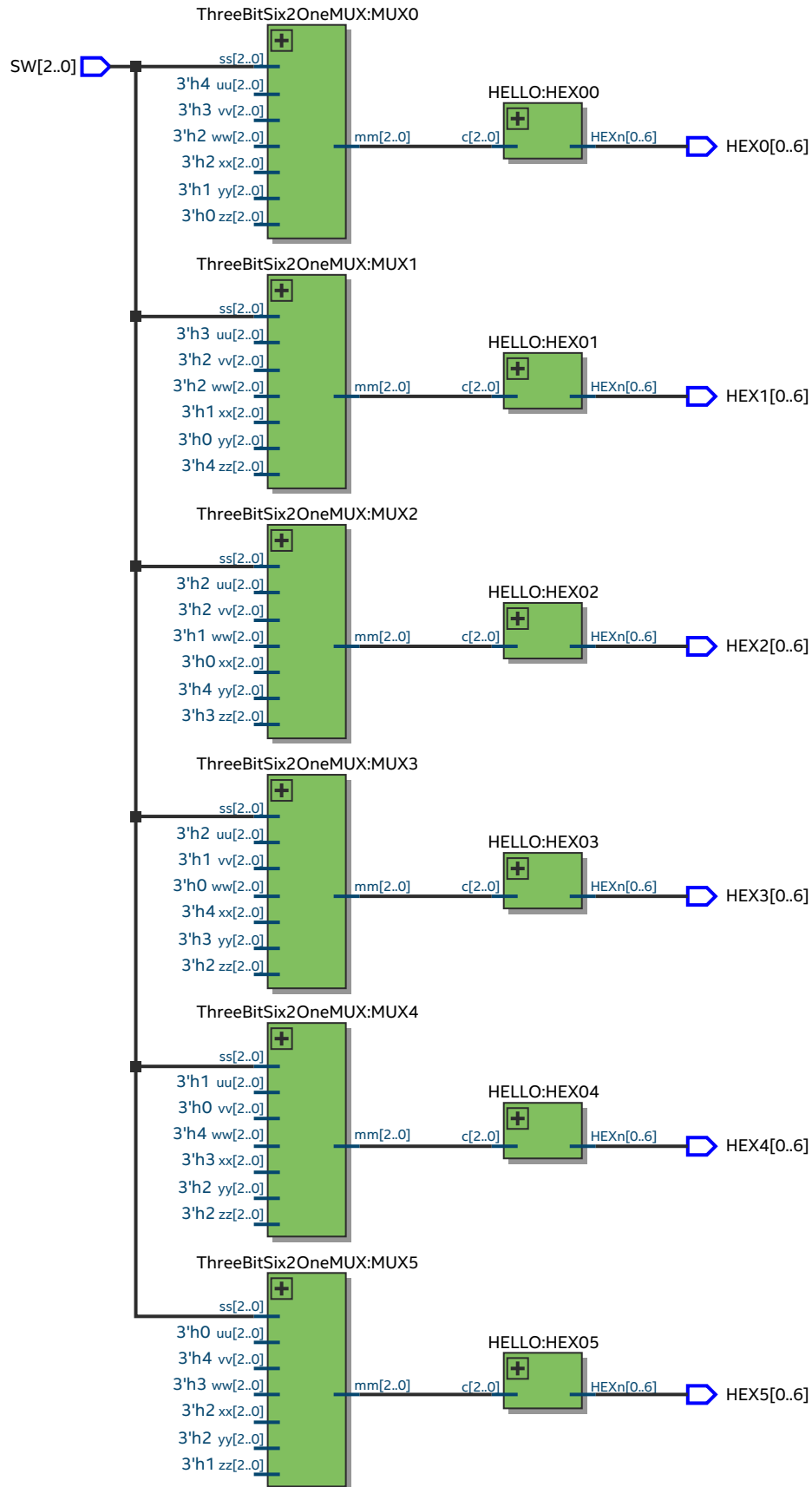

Top level

5. Known how to interface 7-segment LED and multiplexer

v_3	v_2	v_1	v_0	d_1d_0	
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	0	2
0	0	1	1	0	3
0	1	0	0	0	4
0	1	0	1	0	5
0	1	1	0	0	6
0	1	1	1	0	7
1	0	0	0	0	8
1	0	0	1	0	9
1	0	1	0	1	0
1	0	1	1	1	1
1	1	0	0	1	2
1	1	0	1	1	3
1	1	1	0	1	4
1	1	1	1	1	5

a. Method 1: with MUX, comparator and “Circuit A”

Truth tables and functions

Comparator > 9

v_3	v_2	v_1	v_0	z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$\Rightarrow z = v_3(v_2 + v_1)$

Circuit A

v_3	v_2	v_1	v_0	A_3	A_2	A_1	A_0
0	0	0	0	×	×	×	×
0	0	0	1	×	×	×	×
0	0	1	0	×	×	×	×
0	0	1	1	×	×	×	×
0	1	0	0	×	×	×	×
0	1	0	1	×	×	×	×
0	1	1	0	×	×	×	×
0	1	1	1	×	×	×	×
1	0	0	0	×	×	×	×
1	0	0	1	×	×	×	×
1	0	1	0	0	0	0	0
1	0	1	1	0	0	0	1
1	1	0	0	0	0	1	0
1	1	0	1	0	0	1	1
1	1	1	0	0	1	0	0
1	1	1	1	0	1	0	1

\Rightarrow
 $A_3 = 0$
 $A_2 = v_2v_1$
 $A_1 = \bar{v}_1$
 $A_0 = v_0$

Code

BCD.vhdl

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY BCD IS
    PORT (
        c : IN std_logic_vector(3 DOWNTO 0);
        HEXn : OUT std_logic_vector(0 TO 6)
    );
END BCD;

ARCHITECTURE behavior OF BCD IS
    SIGNAL HEX : std_logic_vector(0 TO 6);
BEGIN
    HEXn <= NOT(HEX);
    WITH c SELECT
    HEX <= "1111110" WHEN "0000",
           "0110000" WHEN "0001",
           "1101101" WHEN "0010",
           "1111001" WHEN "0011",
           "0110011" WHEN "0100",
           "1011011" WHEN "0101",
           "1011111" WHEN "0110",
           "1110000" WHEN "0111",
           "1111111" WHEN "1000",
           "1111011" WHEN "1001",
           "0000000" WHEN OTHERS;
END behavior;
```

MUX.vhdl

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY MUX IS
    PORT (
        muxIn1 : IN std_logic;
        muxSel : IN std_logic;
        muxIn2 : IN std_logic;
        muxOut : OUT std_logic
    );
END ENTITY;

ARCHITECTURE arch OF MUX IS
BEGIN
    muxOut <= (NOT(muxSel) AND muxIn1) OR (muxSel AND muxIn2);
END arch;
```

FourBitMUX.vhdl

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY FourBitMUX IS
    PORT (
        fourBitMuxIn1 : IN std_logic_vector(3 DOWNTO 0);
        fourBitMuxIn2 : IN std_logic_vector(3 DOWNTO 0);
        fourBitMuxSel : IN std_logic;
        fourBitMuxOut : OUT std_logic_vector(3 DOWNTO 0)
    );
```

```

END ENTITY;

ARCHITECTURE arch OF FourBitMUX IS
    COMPONENT MUX
        PORT (
            muxIn1 : IN std_logic;
            muxSel  : IN std_logic;
            muxIn2  : IN std_logic;
            muxOut  : OUT std_logic
        );
    END COMPONENT;
BEGIN
    gen : FOR i IN 3 DOWNTO 0 GENERATE
        MUX2 : MUX
            PORT MAP(
                muxSel => fourBitMuxSel,
                muxIn1 => fourBitMuxIn1(i),
                muxIn2 => fourBitMuxIn2(i),
                muxOut => fourBitMuxOut(i)
            );
        END GENERATE;
END arch;

```

Comparator.vhdl

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Comparator IS
    PORT (
        compIn : IN std_logic_vector(3 DOWNTO 0);
        compOut : OUT std_logic
    );
END ENTITY;

ARCHITECTURE behave OF Comparator IS
BEGIN
    --  $Z = A(B+C)$ 
    compOut <= compIn(3) AND (compIn(2) OR compIn(1));

END ARCHITECTURE;

```

CircuitA.vhdl

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY CircuitA IS
    PORT (
        dIn : IN std_logic_vector(3 DOWNTO 0);
        dOut : OUT std_logic_vector(3 DOWNTO 0)
    );
END ENTITY;

ARCHITECTURE behave OF CircuitA IS
BEGIN
    dOut(3) <= '0';
    dOut(2) <= dIn(2) AND dIn(1);
    dOut(1) <= NOT(dIn(1));
    dOut(0) <= dIn(0);

END ARCHITECTURE;

```

Exc5.vhdl

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Exc5 IS
    PORT (
        V : IN std_logic_vector(3 DOWNTO 0);
        HEX0 : OUT std_logic_vector(0 TO 6);
        HEX1 : OUT std_logic_vector(0 TO 6)
    );
END ENTITY;

ARCHITECTURE behave OF Exc5 IS

    SIGNAL z : std_logic;
    SIGNAL A, m : std_logic_vector(3 DOWNTO 0);

    COMPONENT FourBitMUX IS
        PORT (
            fourBitMuxIn1 : IN std_logic_vector(3 DOWNTO 0);
            fourBitMuxIn2 : IN std_logic_vector(3 DOWNTO 0);
            fourBitMuxSel : IN std_logic;
            fourBitMuxOut : OUT std_logic_vector(3 DOWNTO 0)
        );
    END COMPONENT;

    COMPONENT Comparator IS
        PORT (
            compIn : IN std_logic_vector(3 DOWNTO 0);
            compOut : OUT std_logic
        );
    END COMPONENT;

    COMPONENT CircuitA IS
        PORT (
            dIn : IN std_logic_vector(3 DOWNTO 0);
            dOut : OUT std_logic_vector(3 DOWNTO 0)
        );
    END COMPONENT;

    COMPONENT BCD IS
        PORT (
            c : IN std_logic_vector(3 DOWNTO 0);
            HEXn : OUT std_logic_vector(0 TO 6)
        );
    END COMPONENT;


BEGIN
    comp : Comparator PORT MAP( compIn => V, compOut => z);
    cirA : CircuitA PORT MAP(dIn => V, dOut => A);
    mux : FourBitMUX
    PORT MAP(
        fourBitMuxIn1 => V,
        fourBitMuxIn2 => A,
        fourBitMuxSel => z,
        fourBitMuxOut => m
    );

    HEX01 : BCD PORT MAP(c => "000" & z, HEXn => HEX1);
    HEX00 : BCD PORT MAP(c => m, HEXn => HEX0);


END ARCHITECTURE;

```

Result of RTL viewer

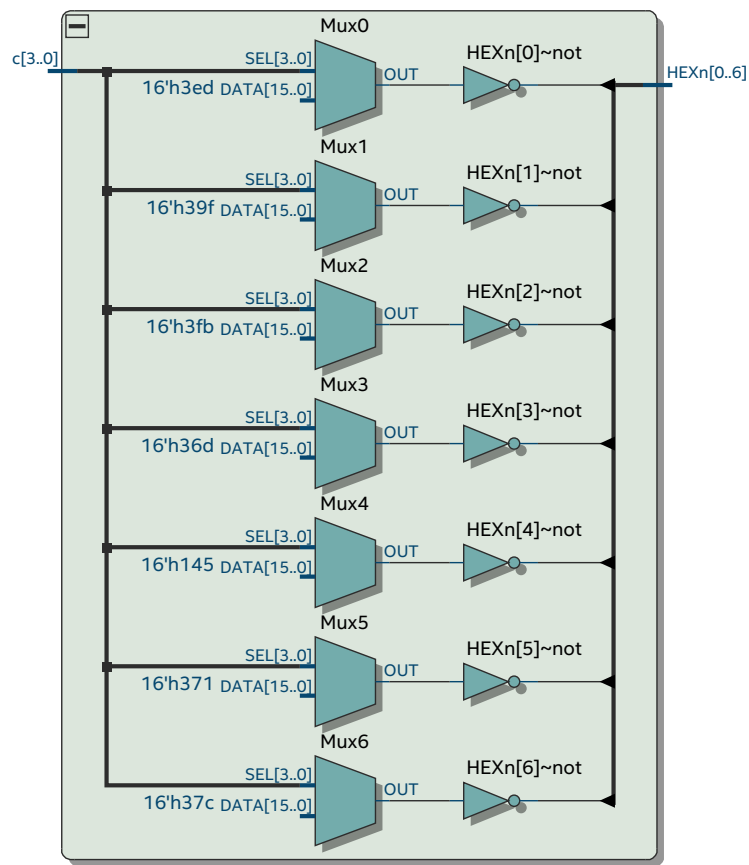


BCD 7-segment decoder

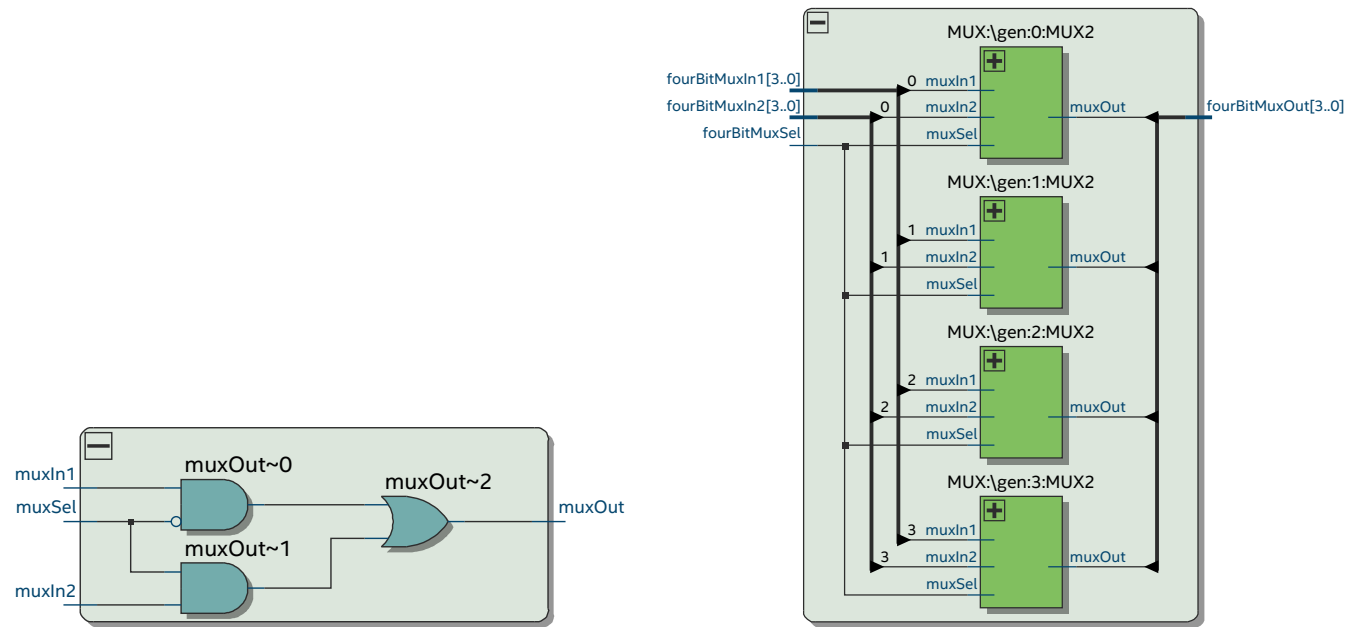


2-to-1 multiplexer


4-bit 2-to-1 multiplexer

 

Comparator > 9

 

Circuit A

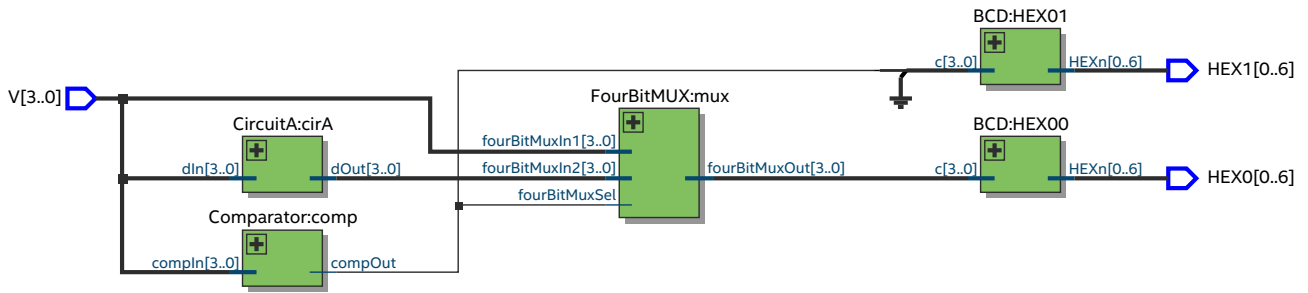

Top level

b. Method 2: using conditions in VHDL

BCD.vhdl

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY BCD IS
    PORT (
        c : IN std_logic_vector(3 DOWNTO 0);
        HEXn : OUT std_logic_vector(0 TO 6)
    );
END BCD;

ARCHITECTURE behavior OF BCD IS
    SIGNAL HEX : std_logic_vector(0 TO 6);
BEGIN
    HEXn <= NOT(HEX);
    WITH c SELECT
    HEX <= "1111110" WHEN "0000",
           "0110000" WHEN "0001",
           "1101101" WHEN "0010",
           "1111001" WHEN "0011",
           "0110011" WHEN "0100",
           "1011011" WHEN "0101",
           "1011111" WHEN "0110",
           "1110000" WHEN "0111",
           "1111111" WHEN "1000",
           "1111011" WHEN "1001",
           "0000000" WHEN OTHERS;
END behavior;

```

Exc5.vhdl

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

```

```

USE IEEE.numeric_std.ALL;

ENTITY Exc5 IS
    PORT (
        V : IN std_logic_vector(3 DOWNT0 0);
        HEX0 : OUT std_logic_vector(0 TO 6);
        HEX1 : OUT std_logic_vector(0 TO 6)
    );
END ENTITY;

ARCHITECTURE behave OF Exc5 IS

    SIGNAL digit1, digit0 : std_logic_vector(3 DOWNT0 0);

    COMPONENT BCD IS
        PORT (
            c : IN std_logic_vector(3 DOWNT0 0);
            HEXn : OUT std_logic_vector(0 TO 6)
        );
    END COMPONENT;


BEGIN
    digit1 <= "0000" WHEN unsigned(V) < 10 ELSE "0001";
    digit0 <= std_logic_vector(unsigned(V) - 10) WHEN unsigned(V) >= 10 ELSE
        std_logic_vector(unsigned(V));

    HEX01 : BCD PORT MAP(c => digit1, HEXn => HEX1);
    HEX00 : BCD PORT MAP(c => digit0, HEXn => HEX0);


END ARCHITECTURE;

```

Result of RTL viewer

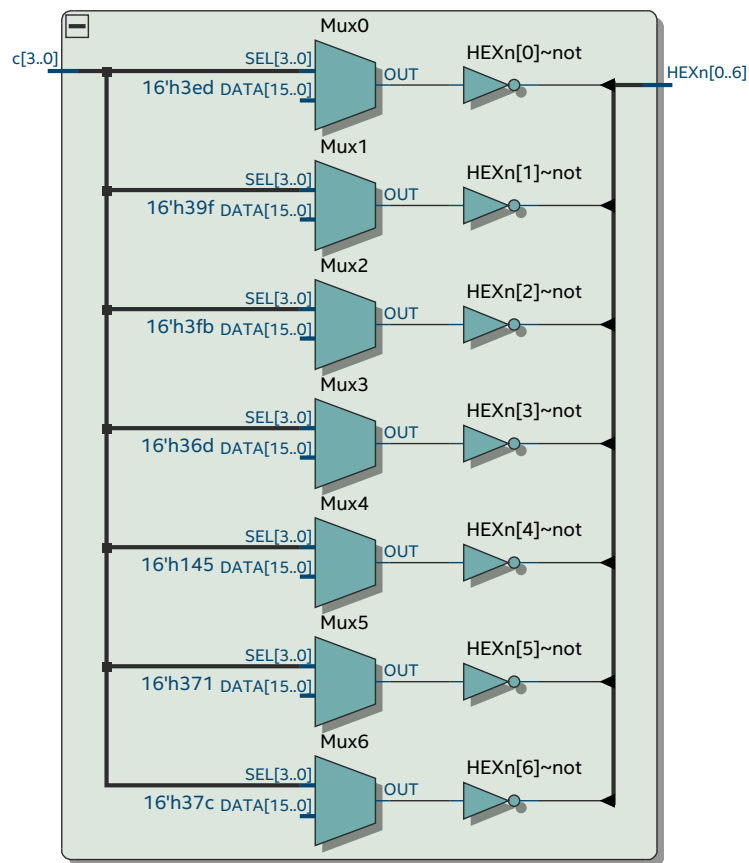

BCD 7-segment decoder

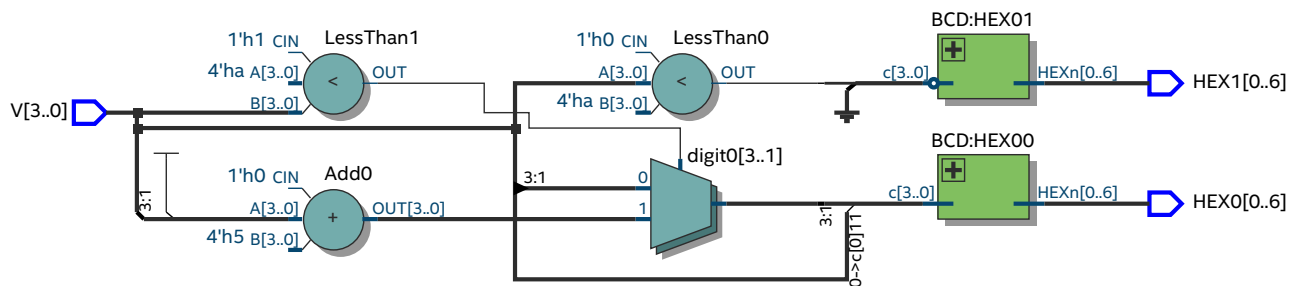

Top level

c. Waveform

