

HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY – VNU HCMC  
OFFICE FOR INTERNATIONAL STUDY PROGRAM  
FACULTY OF ELECTRICAL AND ELECTRONIC ENGINEERING

————— \* —————



## DIGITAL SYSTEMS (LAB) EXPERIMENTAL REPORT (Lab 2)

Lecturer : **Mr. Nguyễn Tuấn Hùng**  
Subject : **Digital Systems**  
Class : **TT06**  
Name : **Lương Triển Thắng**  
Student ID : **2051194**

Ho Chi Minh City, 7<sup>th</sup> June, 2022

# Contents

<b>II</b>	<b>Laboratory 2:</b>	
	<i>Adder and flip-flop</i>	<b>2</b>
1.	Known how to program 4-bit adder . . . . .	2
a.	Code . . . . .	2
b.	Waveform . . . . .	3
c.	Result of RTL viewer . . . . .	3
2.	Known how to program BCD adder . . . . .	4
a.	Code . . . . .	4
b.	Waveform . . . . .	9
c.	Result of RTL viewer . . . . .	10
3.	Known how to program BCD adder . . . . .	13
a.	Code . . . . .	13
b.	Waveform . . . . .	14
c.	Result of RTL viewer . . . . .	14
4.	Known how to program a master-slave D flip-flop . . . . .	15
a.	Code . . . . .	15
b.	Waveform . . . . .	16
c.	Result of RTL viewer . . . . .	16
5.	Known how to program a master-slave D flip-flopCompare the different behavior of the three storage elements: a gated D latch, a positive-edge triggered D flip-flop, and a negative-edge triggered D flip-flop. . . . .	17
a.	Code . . . . .	17
b.	Waveform . . . . .	18
c.	Result of RTL viewer . . . . .	18
6.	Apply all the previous experiments . . . . .	19
a.	Code . . . . .	19
b.	Waveform . . . . .	21
c.	Result of RTL viewer . . . . .	21

# II Laboratory 2

## Adder and flip-flop

### 1. Known how to program 4-bit adder

#### a. Code

##### FA.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Exc1 IS
    PORT (
        a : IN STD_LOGIC;
        b : IN STD_LOGIC;
        ci : IN STD_LOGIC;
        s : OUT STD_LOGIC;
        co : OUT STD_LOGIC
    );
END Exc1;

ARCHITECTURE arch OF Exc1 IS
BEGIN
    s <= a XOR b XOR ci;
    co <= (a AND b) OR (ci AND (a XOR b));
END ARCHITECTURE;
```

##### Exc1.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY Exc1 IS
    PORT (
        an : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        bn : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        cin : IN STD_LOGIC;
        sn : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
        cout : OUT STD_LOGIC
    );
END Exc1;


ARCHITECTURE arch OF Exc1 IS
    SIGNAL cn : STD_LOGIC_VECTOR(4 DOWNTO 1);
    COMPONENT FA IS
        PORT (
            a : IN STD_LOGIC;
            b : IN STD_LOGIC;
            ci : IN STD_LOGIC;
            s : OUT STD_LOGIC;
            co : OUT STD_LOGIC
        );
    END COMPONENT;
BEGIN
    FA0 : FA PORT MAP(
        a => an(0),
```

```


        b => bn(0),
        ci => cin,
        s => sn(0),
        co => cn(1)
    );
    gen : FOR i IN 1 TO 3 GENERATE
        FAn : FA PORT MAP(
            a => an(i),
            b => bn(i),
            ci => cn(i),
            s => sn(i),
            co => cn(i + 1)
        );
    END GENERATE;
    cout <= cn(4);
END ARCHITECTURE;

```


## b. Waveform

 

## c. Result of RTL viewer

 

Full adder

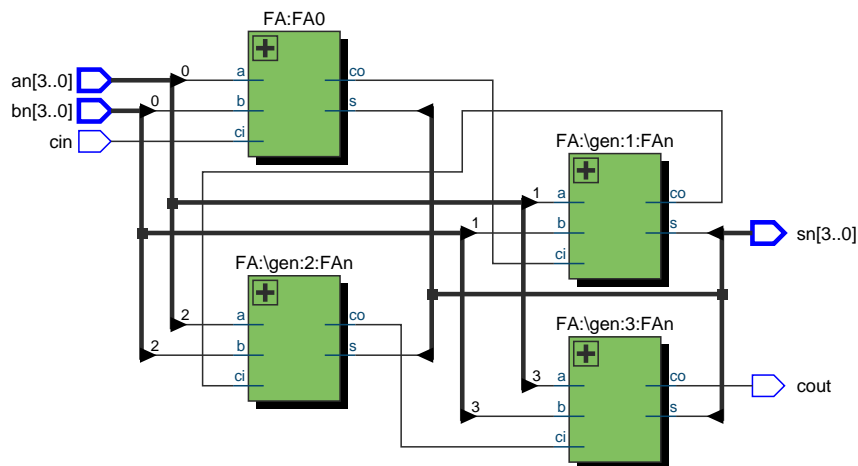

Top level

## 2. Known how to program BCD adder

Comparator > 9

Circuit A

$v_4$	$v_3$	$v_2$	$v_1$	$v_0$	$z$
0	0	0	0	0	0
0	0	0	0	1	0
0	0	0	1	0	0
0	0	0	1	1	0
0	0	1	0	0	0
0	0	1	0	1	0
0	0	1	1	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	0	1	0
0	1	0	1	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	0	0	1	1
1	0	0	1	0	1
1	0	0	1	1	1
1	0	1	0	0	1
1	0	1	0	1	1
1	0	1	1	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	1
1	1	0	1	0	1
1	1	0	1	1	1
1	1	1	0	0	1
1	1	1	0	1	1
1	1	1	1	0	1
1	1	1	1	1	1

$$\Rightarrow z = v_3(v_2 + v_1)$$

$v_4$	$v_3$	$v_2$	$v_1$	$v_0$	$A_4$	$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	×	×	×	×	×
0	0	0	0	1	×	×	×	×	×
0	0	0	1	0	×	×	×	×	×
0	0	0	1	1	×	×	×	×	×
0	0	1	0	0	×	×	×	×	×
0	0	1	0	1	×	×	×	×	×
0	0	1	1	0	×	×	×	×	×
0	0	1	1	1	×	×	×	×	×
0	1	0	0	0	×	×	×	×	×
0	1	0	0	1	×	×	×	×	×
0	1	0	1	0	0	0	0	0	0
0	1	0	1	1	0	0	0	0	1
0	1	1	0	0	0	0	0	1	0
0	1	1	0	1	0	0	0	1	1
0	1	1	1	0	0	0	1	0	0
0	1	1	1	1	0	0	1	0	1
1	0	0	0	0	0	0	1	1	0
1	0	0	0	1	0	0	1	1	1
1	0	0	1	0	0	1	0	0	0
1	0	0	1	1	0	1	0	0	1
1	0	1	0	0	×	×	×	×	×
1	0	1	0	1	×	×	×	×	×
1	0	1	1	0	×	×	×	×	×
1	0	1	1	1	×	×	×	×	×
1	1	0	0	0	×	×	×	×	×
1	1	0	0	1	×	×	×	×	×
1	1	0	1	0	×	×	×	×	×
1	1	0	1	1	×	×	×	×	×
1	1	1	0	0	×	×	×	×	×
1	1	1	0	1	×	×	×	×	×
1	1	1	1	0	×	×	×	×	×
1	1	1	1	1	×	×	×	×	×

$$\begin{aligned} A_4 &= 0 \\ A_3 &= \overline{v_3}v_1 \\ \Rightarrow A_2 &= \overline{v_2} \oplus v_1 \\ A_1 &= \overline{v_1} \\ A_0 &= v_0 \end{aligned}$$

### a. Code

MUX.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY MUX IS
    PORT (
        muxIn1 : IN STD_LOGIC;
        muxSel  : IN STD_LOGIC;
        muxIn2 : IN STD_LOGIC;
        muxOut  : OUT STD_LOGIC
    );
END ENTITY;

ARCHITECTURE arch OF MUX IS
BEGIN
    muxOut <= (NOT(muxSel) AND muxIn1) OR (muxSel AND muxIn2);
END arch;

```

## FourBitMUX.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY FourBitMUX IS
    PORT (
        fourBitMuxIn1 : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
        fourBitMuxIn2 : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
        fourBitMuxSel : IN STD_LOGIC;
        fourBitMuxOut : OUT STD_LOGIC_VECTOR(4 DOWNTO 0)
    );
END ENTITY;

ARCHITECTURE arch OF FourBitMUX IS
    COMPONENT MUX
        PORT (
            muxIn1 : IN STD_LOGIC;
            muxSel : IN STD_LOGIC;
            muxIn2 : IN STD_LOGIC;
            muxOut : OUT STD_LOGIC
        );
    END COMPONENT;
BEGIN
    gen : FOR i IN 4 DOWNTO 0 GENERATE
        MUX2 : MUX PORT MAP(
            muxSel => fourBitMuxSel,
            muxIn1 => fourBitMuxIn1(i),
            muxIn2 => fourBitMuxIn2(i),
            muxOut => fourBitMuxOut(i)
        );
    END GENERATE;
END arch;
```

## Comparator.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Comparator IS
    PORT (
        compIn : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
        compOut : OUT STD_LOGIC
    );
END ENTITY;

ARCHITECTURE behave OF Comparator IS
BEGIN
    --  $Z = A+B(C+D)$ 
    compOut <= compIn(4) OR (compIn(3) AND (compIn(2) OR compIn(1)));
END ARCHITECTURE;
```

## CircuitA.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY CircuitA IS
    PORT (
        dIn : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
        dOut : OUT STD_LOGIC_VECTOR(4 DOWNTO 0)
    );
END ENTITY;
```

```

ARCHITECTURE behave OF CircuitA IS
BEGIN
    --  $V = 0$ 
    dOut(4) <= '0';

    --  $W = B'D$ 
    dOut(3) <= NOT(dIn(3)) AND dIn(1);

    --  $Y = C'D' + CD$ 
    dOut(2) <= dIn(2) XNOR dIn(1);

    --  $X = D'$ 
    dOut(1) <= NOT(dIn(1));

    --  $Z = E$ 
    dOut(0) <= dIn(0);

END ARCHITECTURE;

```

## BCD.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY BCD IS
    PORT (
        c : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
        HEXn : OUT STD_LOGIC_VECTOR(0 TO 6)
    );
END BCD;

ARCHITECTURE behavior OF BCD IS
    SIGNAL HEX : STD_LOGIC_VECTOR(0 TO 6);
BEGIN
    HEXn <= NOT(HEX);
    WITH c SELECT
        HEX <= "111110" WHEN "00000",
               "0110000" WHEN "00001",
               "1101101" WHEN "00010",
               "1111001" WHEN "00011",
               "0110011" WHEN "00100",
               "1011011" WHEN "00101",
               "1011111" WHEN "00110",
               "1110000" WHEN "00111",
               "1111111" WHEN "01000",
               "1111011" WHEN "01001",
               "0000000" WHEN OTHERS;
END behavior;

```

## BCDDisplay.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY BCDDisplay IS
    PORT (
        V : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
        HEX0 : OUT STD_LOGIC_VECTOR(0 TO 6);
        HEX1 : OUT STD_LOGIC_VECTOR(0 TO 6)
    );
END ENTITY;

```

```
ARCHITECTURE behave OF BCDDisplay IS
```

```

    SIGNAL z : STD_LOGIC;
    SIGNAL A, m : STD_LOGIC_VECTOR(4 DOWNTO 0);

    COMPONENT FourBitMUX IS
        PORT (
            fourBitMuxIn1 : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
            fourBitMuxIn2 : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
            fourBitMuxSel : IN STD_LOGIC;
            fourBitMuxOut : OUT STD_LOGIC_VECTOR(4 DOWNTO 0)
        );
    END COMPONENT;
```

```

    COMPONENT Comparator IS
        PORT (
            compIn : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
            compOut : OUT STD_LOGIC
        );
    END COMPONENT;
```

```

    COMPONENT CircuitA IS
        PORT (
            dIn : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
            dOut : OUT STD_LOGIC_VECTOR(4 DOWNTO 0)
        );
    END COMPONENT;
```

```

    COMPONENT BCD IS
        PORT (
            c : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
            HEXn : OUT STD_LOGIC_VECTOR(0 TO 6)
        );
    END COMPONENT;
```

```
BEGIN
```

```

    comp : Comparator PORT MAP(
        compIn => V,
        compOut => z
    );
```

```

    cirA : CircuitA PORT MAP(
        dIn => V,
        dOut => A
    );
```

```

    mux : FourBitMUX PORT MAP(
        fourBitMuxIn1 => V,
        fourBitMuxIn2 => A,
        fourBitMuxSel => z,
        fourBitMuxOut => m
    );
```

```

    HEX01 : BCD PORT MAP(c => "0000" & z, HEXn => HEX1);
    HEX00 : BCD PORT MAP(c => m, HEXn => HEX0);
```

```
END ARCHITECTURE;
```

FA.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
```

```
ENTITY Exc1 IS
```



```

        PORT (
            a : IN STD_LOGIC;
            b : IN STD_LOGIC;
            ci : IN STD_LOGIC;
            s : OUT STD_LOGIC;
            co : OUT STD_LOGIC
        );
END Exc1;

ARCHITECTURE arch OF Exc1 IS
BEGIN
    s <= a XOR b XOR ci;
    co <= (a AND b) OR (ci AND (a XOR b));
END ARCHITECTURE;

```

## Exc2.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY Exc2 IS
    PORT (
        an : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        bn : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        cin : IN STD_LOGIC;
        HEXo0 : OUT STD_LOGIC_VECTOR(0 TO 6);
        HEXo1 : OUT STD_LOGIC_VECTOR(0 TO 6);
        HEXo3 : OUT STD_LOGIC_VECTOR(0 TO 6);
        HEXo5 : OUT STD_LOGIC_VECTOR(0 TO 6);
        error : OUT STD_LOGIC;
        sum : OUT STD_LOGIC_VECTOR(4 DOWNTO 0)
    );
END ENTITY;

ARCHITECTURE arch OF Exc2 IS
    SIGNAL cn : STD_LOGIC_VECTOR(4 DOWNTO 1);
    SIGNAL sn : STD_LOGIC_VECTOR(4 DOWNTO 0);
    SIGNAL errorA, errorB : STD_LOGIC;
    COMPONENT FA IS
        PORT (
            a : IN STD_LOGIC;
            b : IN STD_LOGIC;
            ci : IN STD_LOGIC;
            s : OUT STD_LOGIC;
            co : OUT STD_LOGIC
        );
    END COMPONENT;

    COMPONENT BCDDisplay IS
        PORT (
            V : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
            HEX0 : OUT STD_LOGIC_VECTOR(0 TO 6);
            HEX1 : OUT STD_LOGIC_VECTOR(0 TO 6)
        );
    END COMPONENT;

    COMPONENT BCD IS
        PORT (
            c : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
            HEXn : OUT STD_LOGIC_VECTOR(0 TO 6)
        );
    END COMPONENT;

```

```

COMPONENT Comparator IS
    PORT (
        compIn : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
        compOut : OUT STD_LOGIC
    );
END COMPONENT;

BEGIN

HEX5 : BCD PORT MAP(c => '0' & an, HEXn => HEXo5);
HEX3 : BCD PORT MAP(c => '0' & bn, HEXn => HEXo3);

FA0 : FA PORT MAP(
    a => an(0),
    b => bn(0),
    ci => cin,
    s => sn(0),
    co => cn(1)
);

gen : FOR i IN 1 TO 3 GENERATE
    FAn : FA PORT MAP(
        a => an(i),
        b => bn(i),
        ci => cn(i),
        s => sn(i),
        co => cn(i + 1)
    );
END GENERATE;


sn(4) <= cn(4);
sum <= sn;

BCDHEX : BCDDisplay PORT MAP(V => sn, HEX0 => HEXo0, HEX1 => HEXo1);
errorLED0 : Comparator PORT MAP(compIn => '0' & an, compOut => errorA);
errorLED1 : Comparator PORT MAP(compIn => '0' & bn, compOut => errorB);


error <= errorA OR errorB;
END ARCHITECTURE;

```


## b. Waveform

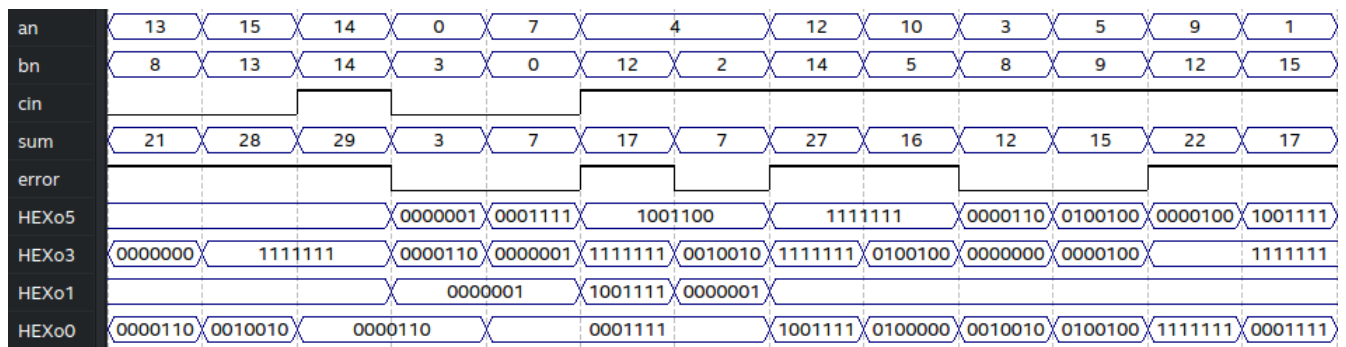


c. Result of RTL viewer

 


MUX

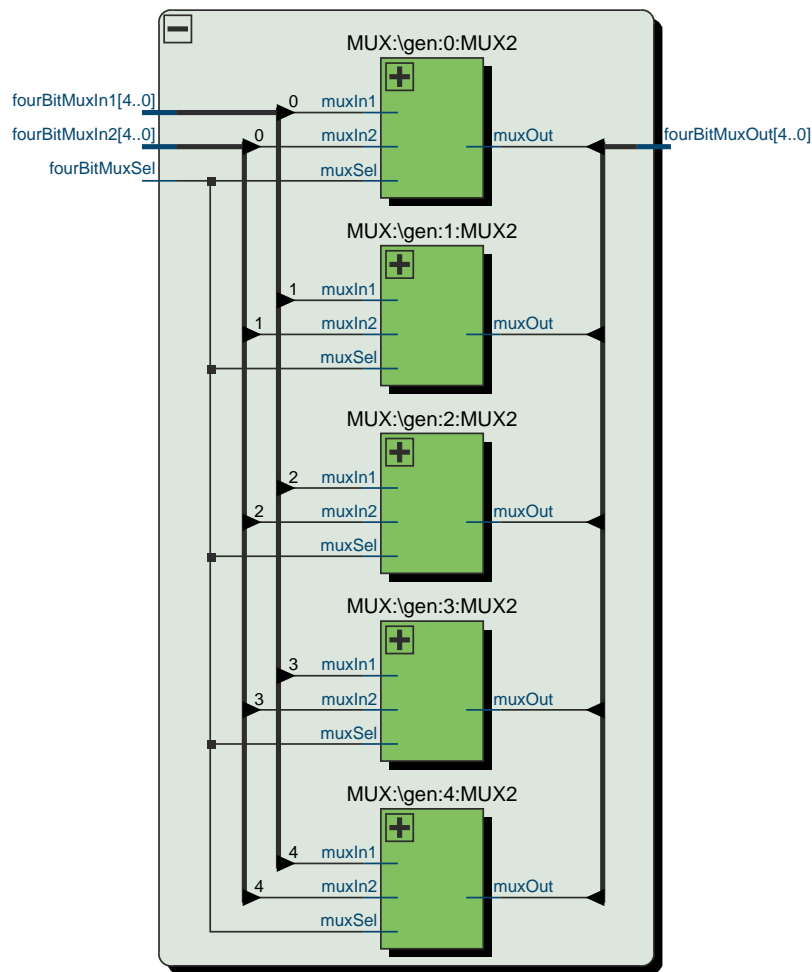


4-bit MUX

 


Comparator

 


CircuitA

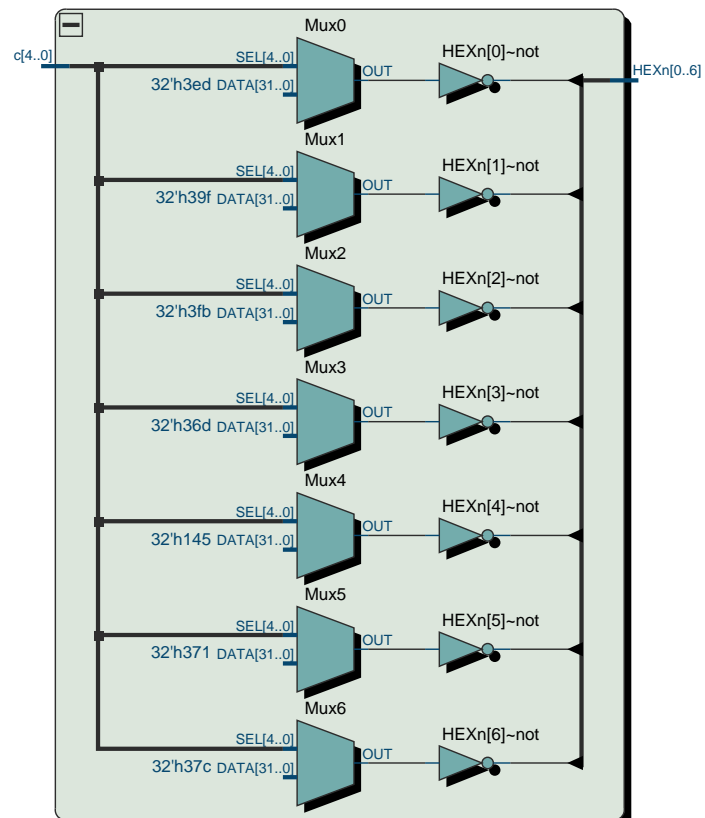


BCD MUX

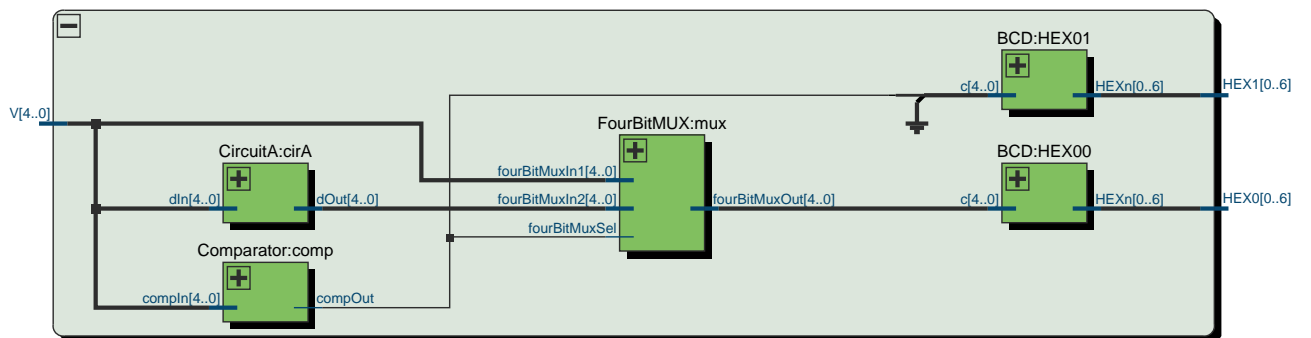

BCD Decoder

 

Full adder

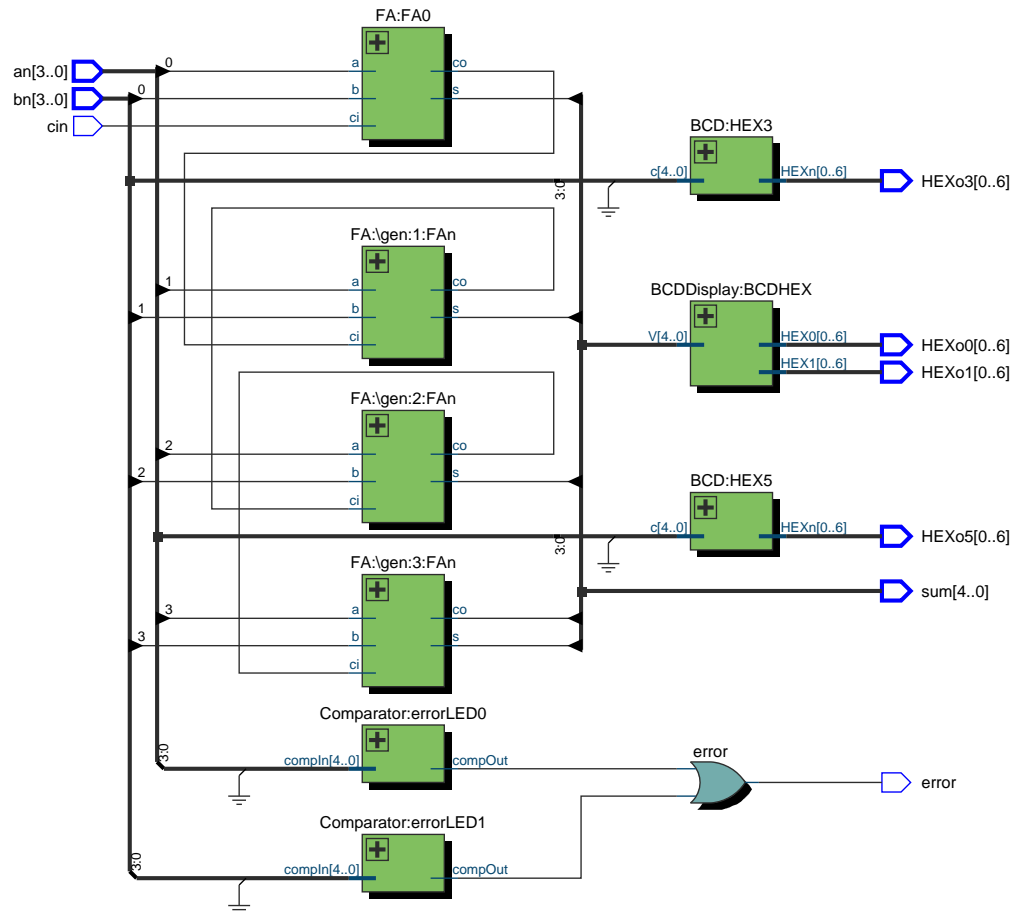

Top level

### 3. Known how to program BCD adder

#### a. Code

##### BCD.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY BCD IS
    PORT (
        c : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
        HEXn : OUT STD_LOGIC_VECTOR(0 TO 6)
    );
END BCD;

ARCHITECTURE behavior OF BCD IS
    SIGNAL HEX : STD_LOGIC_VECTOR(0 TO 6);
BEGIN
    HEXn <= NOT(HEX);
    WITH c SELECT
        HEX <= "1111110" WHEN "00000",
        "0110000" WHEN "00001",
        "1101101" WHEN "00010",
        "1111001" WHEN "00011",
        "0110011" WHEN "00100",
        "1011011" WHEN "00101",
        "1011111" WHEN "00110",
        "1110000" WHEN "00111",
        "1111111" WHEN "01000",
        "1111011" WHEN "01001",
        "0000000" WHEN OTHERS;
END behavior;
```

##### Exc3.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY Exc3 IS
    PORT (
        an : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        bn : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        cin : IN STD_LOGIC_VECTOR(0 DOWNTO 0);
        HEXo0 : OUT STD_LOGIC_VECTOR(0 TO 6);
        HEXo1 : OUT STD_LOGIC_VECTOR(0 TO 6);
        HEXo3 : OUT STD_LOGIC_VECTOR(0 TO 6);
        HEXo5 : OUT STD_LOGIC_VECTOR(0 TO 6);
        sum : OUT STD_LOGIC_VECTOR(4 DOWNTO 0);
        error : OUT STD_LOGIC
    );
END ENTITY;

ARCHITECTURE arch OF Exc3 IS
    SIGNAL sn : STD_LOGIC_VECTOR(4 DOWNTO 0);
    SIGNAL digit1, digit0 : STD_LOGIC_VECTOR(4 DOWNTO 0);

    COMPONENT BCD IS
        PORT (
            c : IN STD_LOGIC_VECTOR(4 DOWNTO 0);
            HEXn : OUT STD_LOGIC_VECTOR(0 TO 6)
        );
    END COMPONENT;
```

```

END COMPONENT;

BEGIN
  HEX5 : BCD PORT MAP(c => '0' & an, HEXn => HEXo5);
  HEX3 : BCD PORT MAP(c => '0' & bn, HEXn => HEXo3);

  sn <= STD_LOGIC_VECTOR(unsigned('0' & an) + unsigned('0' & bn) + unsigned(cin));
  digit1 <= STD_LOGIC_VECTOR(unsigned(sn) / 10);
  digit0 <= STD_LOGIC_VECTOR(unsigned(sn) MOD 10);


  HEX01 : BCD PORT MAP(c => digit1, HEXn => HEXo1);
  HEX00 : BCD PORT MAP(c => digit0, HEXn => HEXo0);

  sum <= sn;


  error <= '1' WHEN (unsigned(an) > 9 OR unsigned(bn) > 9) ELSE '0';
END ARCHITECTURE;

```


## b. Waveform

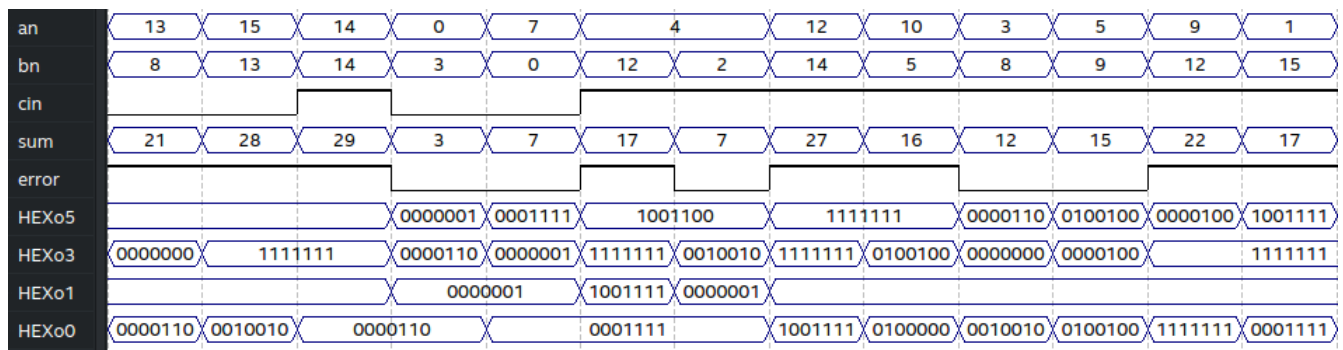

## c. Result of RTL viewer

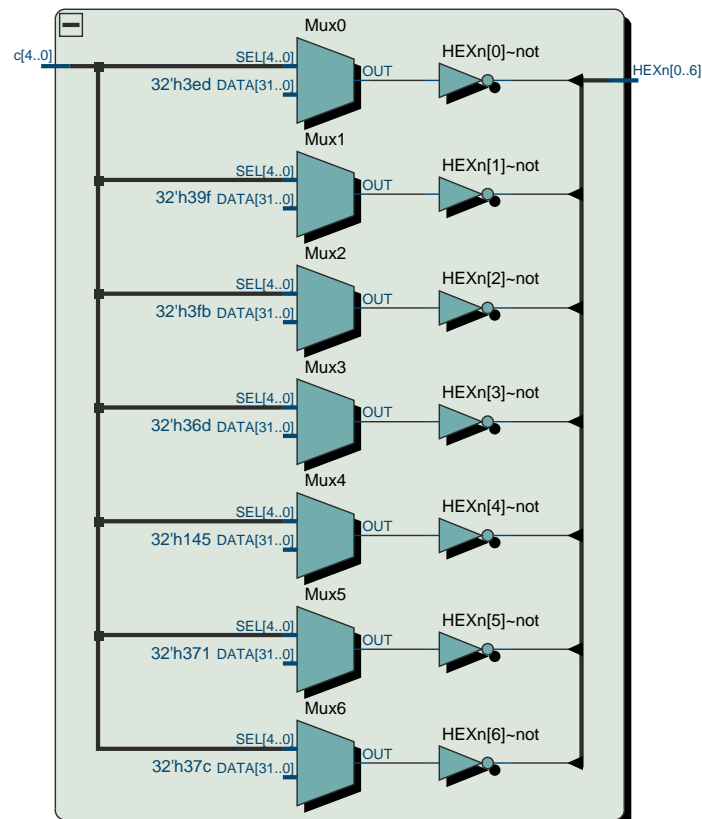

BCD MUX

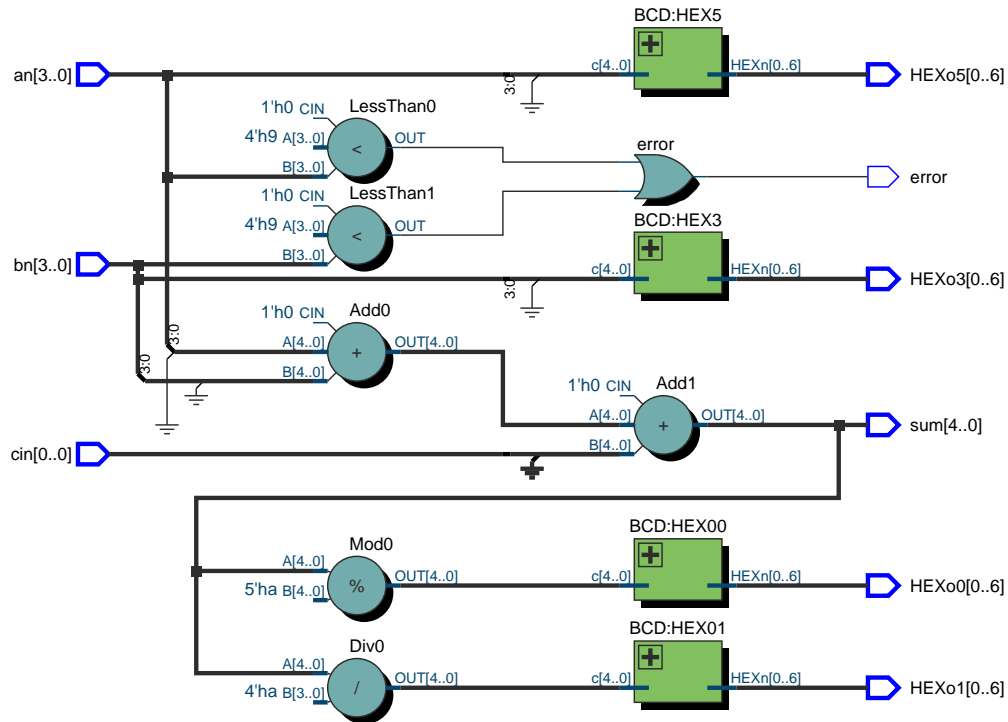

Top level

The circuit is simpler when relying more on the VHDL compiler.

#### 4. Known how to program a master-slave D flip-flop

##### a. Code

###### DFFn.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY DFFn IS
    PORT (
        DClk, Din : IN STD_LOGIC;
        DQ : OUT STD_LOGIC
    );
END DFFn;

ARCHITECTURE Structural OF DFFn IS
    SIGNAL R_g, S_g, Qa, Qb, S, R : STD_LOGIC;
    ATTRIBUTE KEEP : BOOLEAN;
    ATTRIBUTE KEEP OF R_g, S_g, Qa, Qb : SIGNAL IS TRUE;

BEGIN
    S <= Din;
    R <= NOT(Din);
    R_g <= R AND DClk;
    S_g <= S AND DClk;
    Qa <= R_g NOR Qb;
    Qb <= S_g NOR Qa;
    DQ <= Qa;
END Structural;

```



## Exc4.vhd

```


LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Exc4 IS
    PORT (
        D, Clk : IN STD_LOGIC;
        Q : OUT STD_LOGIC
    );
END Exc4;


ARCHITECTURE arch OF Exc4 IS
    SIGNAL Qm : STD_LOGIC;
    COMPONENT DFFn IS
        PORT (
            DClk, Din : IN STD_LOGIC;
            DQ : OUT STD_LOGIC
        );
    END COMPONENT;
BEGIN
    DFF1 : DFFn PORT MAP(DClk => NOT(Clk), Din => D, DQ => Qm);
    DFF0 : DFFn PORT MAP(DClk => Clk, Din => Qm, DQ => Q);
END ARCHITECTURE;

```


## b. Waveform

 

## c. Result of RTL viewer

 

D flip-flop

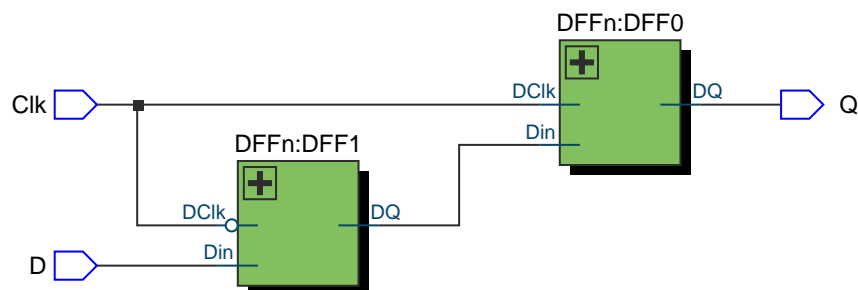

Top level

5. Known how to program a master-slave D flip-flop Compare the different behavior of the three storage elements: a gated D latch, a positive-edge triggered D flip-flop, and a negative-edge triggered D flip-flop.

a. Code

DL.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY DL IS
    PORT (
        DLin, DLClk : IN STD_LOGIC;
        DLQ : OUT STD_LOGIC);
END DL;
ARCHITECTURE Behavior OF DL IS
BEGIN
    PROCESS (DLin, DLClk)
    BEGIN
        IF DLClk = '1' THEN
            DLQ <= DLin;
        END IF;
    END PROCESS;
END Behavior;
```

DFFn.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY DFFn IS
    PORT (
        DClk, Din : IN STD_LOGIC;
        DQ : OUT STD_LOGIC
    );
END DFFn;

ARCHITECTURE Structural OF DFFn IS
BEGIN
    PROCESS (DClk)
    BEGIN
        IF rising_edge(DClk) THEN
            DQ <= Din;
        END IF;
    END PROCESS;
END Structural;
```

Exc5.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY Exc5 IS
    PORT (
        D, Clk : IN STD_LOGIC;
        Qa, Qb, Qc : OUT STD_LOGIC
    );
END Exc5;

ARCHITECTURE arch OF Exc5 IS
    COMPONENT DL IS
```

```


        PORT (
            DLin, DLClk : IN STD_LOGIC;
            DLQ : OUT STD_LOGIC);
    END COMPONENT;

    COMPONENT DFFn IS
        PORT (
            Din, DClk : IN STD_LOGIC;
            DQ : OUT STD_LOGIC);
    END COMPONENT;


BEGIN
    DFF2 : DL PORT MAP(DLin => D, DLClk => Clk, DLQ => Qa);
    DFF1 : DFFn PORT MAP(Din => D, DClk => Clk, DQ => Qb);
    DFF0 : DFFn PORT MAP(Din => D, DClk => NOT(Clk), DQ => Qc);
END ARCHITECTURE;

```


## b. Waveform

 


## c. Result of RTL viewer

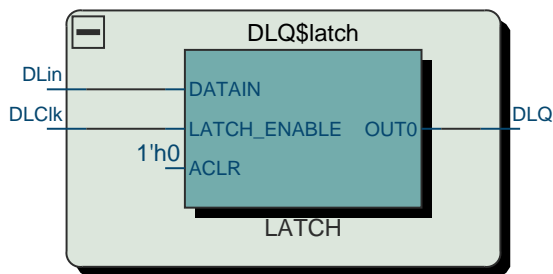

D latch

 

D flip-flop

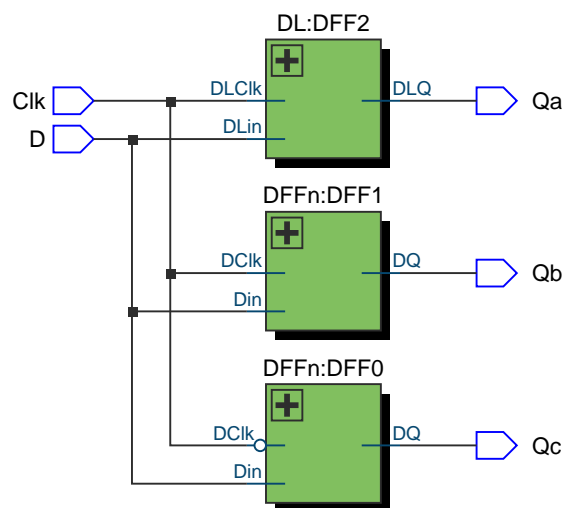

Top level

## 6. Apply all the previous experiments

### a. Code

#### DFFn.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY DFFn IS
    PORT (
        Din, DClk, Drst : IN STD_LOGIC;
        DQ : OUT STD_LOGIC);
END DFFn;
ARCHITECTURE Behavior OF DFFn IS
BEGIN
    PROCESS (Drst, DClk)
    BEGIN
        IF rising_edge(DClk) THEN
            DQ <= Din;
        END IF;
        IF Drst = '1' THEN
            DQ <= '0';
        END IF;
    END PROCESS;
END Behavior;
```

#### EightBitReg.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY EightBitReg IS
    PORT (
        EBRClk, EBRrst : IN STD_LOGIC;
        EBRD : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
        EBRQ : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)
    );
END EightBitReg;

ARCHITECTURE arch OF EightBitReg IS
    COMPONENT DFFn IS
        PORT (
            Din, DClk, Drst : IN STD_LOGIC;
            DQ : OUT STD_LOGIC);
    END COMPONENT;
BEGIN
    gen : FOR i IN 7 DOWNTO 0 GENERATE
        DFFs : DFFn PORT MAP(Din => EBRD(i), DClk => EBRClk, Drst => EBRrst, DQ => EBRQ(i));
    END GENERATE;
END ARCHITECTURE;
```

#### HEXDisplay.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY HEXDisplay IS
    PORT (
        c : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        HEXn : OUT STD_LOGIC_VECTOR(0 TO 6)
    );
END HEXDisplay;
```

```

ARCHITECTURE behavior OF HEXDisplay IS
    SIGNAL HEX : STD_LOGIC_VECTOR(0 TO 6);
BEGIN
    HEXn <= NOT(HEX);
    WITH c SELECT
        HEX <= "1111110" WHEN "0000",
        "0110000" WHEN "0001",
        "1101101" WHEN "0010",
        "1111001" WHEN "0011",
        "0110011" WHEN "0100",
        "1011011" WHEN "0101",
        "1011111" WHEN "0110",
        "1110000" WHEN "0111",
        "1111111" WHEN "1000",
        "1111011" WHEN "1001",

        "1110111" WHEN "1010",
        "0011111" WHEN "1011",
        "1001110" WHEN "1100",
        "0111101" WHEN "1101",
        "1001111" WHEN "1110",
        "1000111" WHEN "1111",
        "0000000" WHEN OTHERS;
END behavior; -- behavior

```

## Exc6.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY Exc6 IS
    PORT (
        ClkN, rstN : IN STD_LOGIC;
        D : IN STD_LOGIC_VECTOR(7 DOWNT0 0);
        cout : OUT STD_LOGIC;
        HEX5 : OUT STD_LOGIC_VECTOR(0 TO 6);
        HEX4 : OUT STD_LOGIC_VECTOR(0 TO 6);
        HEX3 : OUT STD_LOGIC_VECTOR(0 TO 6);
        HEX2 : OUT STD_LOGIC_VECTOR(0 TO 6);
        HEX1 : OUT STD_LOGIC_VECTOR(0 TO 6);
        HEX0 : OUT STD_LOGIC_VECTOR(0 TO 6)
    );
END Exc6;

ARCHITECTURE arch OF Exc6 IS
    SIGNAL sum : STD_LOGIC_VECTOR(8 DOWNT0 0);
    SIGNAL Q : STD_LOGIC_VECTOR(7 DOWNT0 0);
    SIGNAL Clk, rst : STD_LOGIC;
    COMPONENT EightBitReg IS
        PORT (
            EBRClk, EBRrst : IN STD_LOGIC;
            EBRD : IN STD_LOGIC_VECTOR(7 DOWNT0 0);
            EBRQ : OUT STD_LOGIC_VECTOR(7 DOWNT0 0)
        );
    END COMPONENT;

    COMPONENT HEXDisplay IS
        PORT (
            c : IN STD_LOGIC_VECTOR(3 DOWNT0 0);
            HEXn : OUT STD_LOGIC_VECTOR(0 TO 6)
        );
    END COMPONENT;

```


```

END COMPONENT;


BEGIN
    Clk <= NOT(ClkN);
    rst <= NOT(rstN);
    sum <= STD_LOGIC_VECTOR(unsigned('0' & Q) + unsigned('0' & D));
    EBR : EightBitReg PORT MAP(EBRClk => Clk, EBRrst => rst, EBRD => D, EBRQ => Q);
    HEX05 : HEXDisplay PORT MAP(c => sum(7 DOWNTO 4), HEXn => HEX5);
    HEX04 : HEXDisplay PORT MAP(c => sum(3 DOWNTO 0), HEXn => HEX4);
    HEX03 : HEXDisplay PORT MAP(c => D(7 DOWNTO 4), HEXn => HEX3);
    HEX02 : HEXDisplay PORT MAP(c => D(3 DOWNTO 0), HEXn => HEX2);
    HEX01 : HEXDisplay PORT MAP(c => Q(7 DOWNTO 4), HEXn => HEX1);
    HEX00 : HEXDisplay PORT MAP(c => Q(3 DOWNTO 0), HEXn => HEX0);
    cout <= sum(8);
END ARCHITECTURE;


```

## b. Waveform

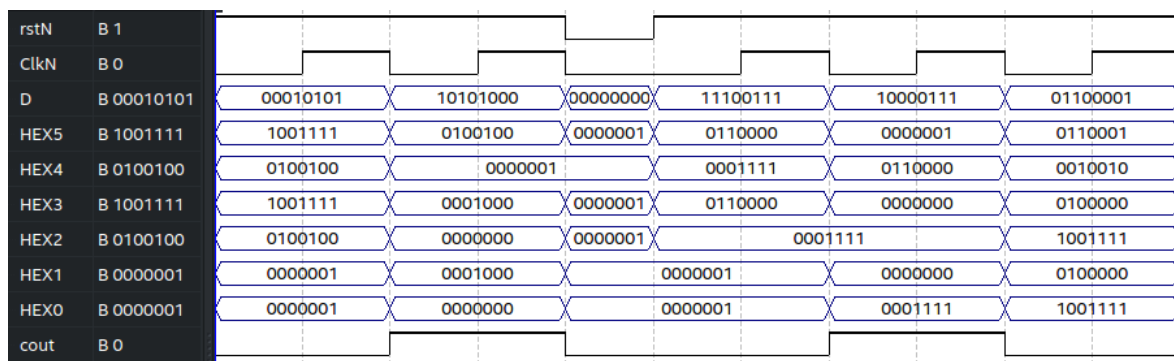


## c. Result of RTL viewer

 

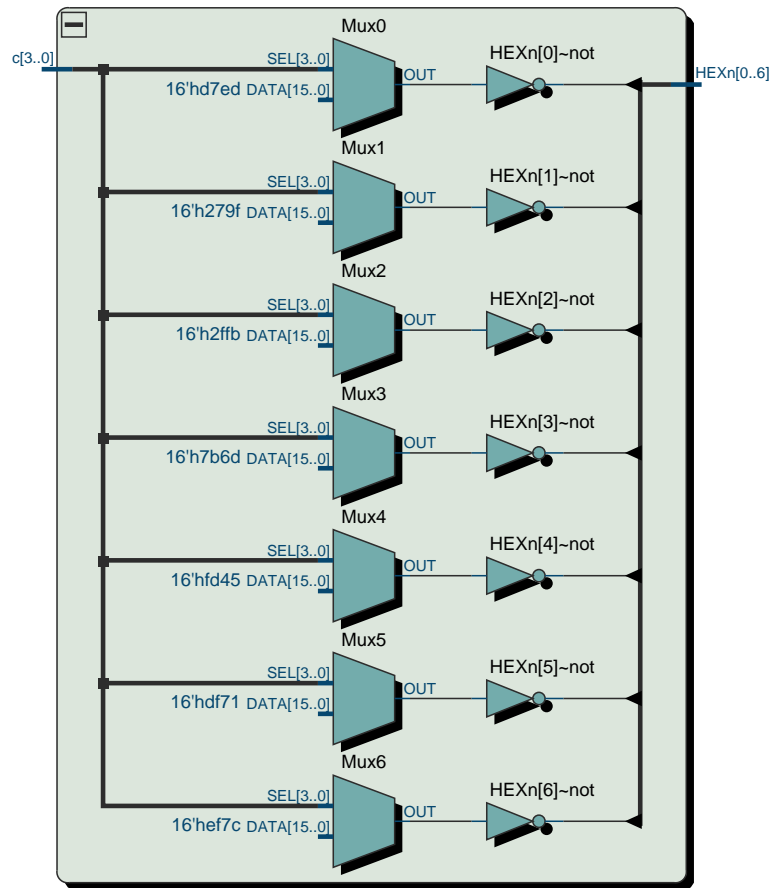

HEX display decoder

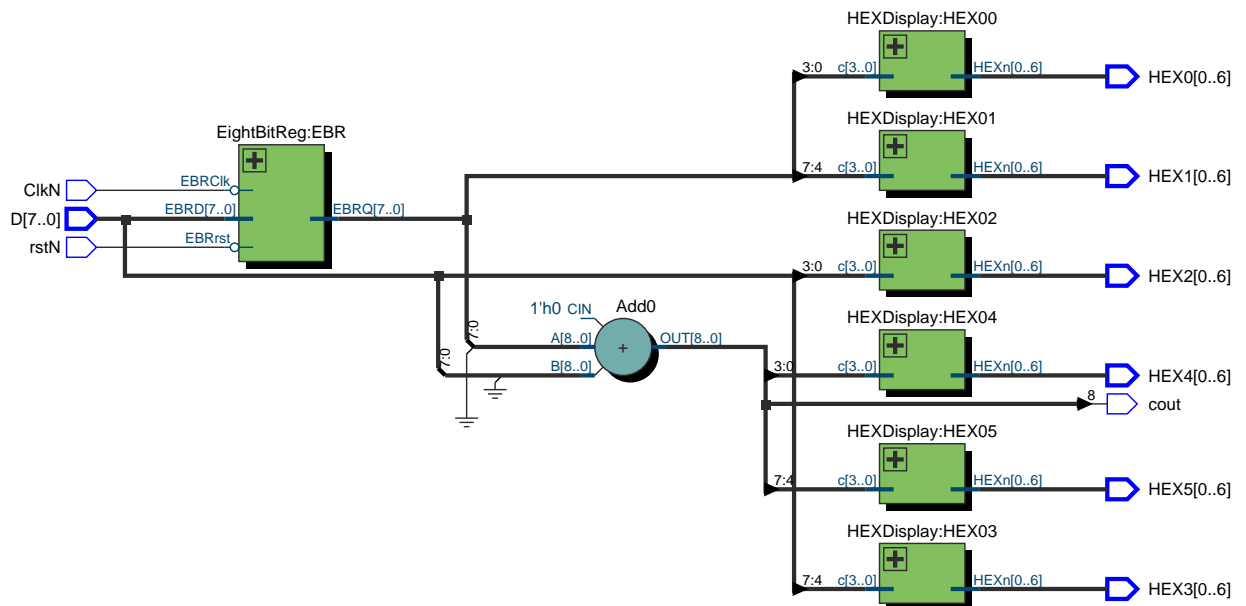

Top level