

HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY – VNU HCMC
OFFICE FOR INTERNATIONAL STUDY PROGRAM
FACULTY OF ELECTRICAL AND ELECTRONIC ENGINEERING

————— * —————



DIGITAL SYSTEMS (LAB) EXPERIMENTAL REPORT (Lab 0)

Lecturer : **Mr. Nguyễn Tuấn Hùng**
Subject : **Digital Systems**
Class : **TT06**
Name : **Lương Triển Thắng**
Student ID : **2051194**

Ho Chi Minh City, 31st May, 2022

Contents

Laboratory 0:	
<i>VHDL Description</i>	2
1. Write VHDL code to describe a digital circuit	2
a. Code	2
b. Waveform	2
c. Result of RTL viewer	3
2. Write VHDL code to describe a truth table	3
a. Code	3
b. Waveform	4
c. Result of RTL viewer	4

Laboratory 0

VHDL Description

1. Write VHDL code to describe a digital circuit


 


Figure 0.1.a: Circuit diagram


a. Code

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY Exc1 IS
    PORT (
        Y3, Y2, Y1, Y0 : IN STD_LOGIC;
        A1, A0, V : OUT STD_LOGIC
    );
END Exc1;
ARCHITECTURE Logic OF Exc1 IS
BEGIN
    A1 <= Y3 OR Y2;
    A0 <= Y3 OR (NOT(Y2) AND Y1);
    V <= Y0 OR Y1 OR Y2 OR Y3;
END Logic;
```

b. Waveform

 

c. Result of RTL viewer

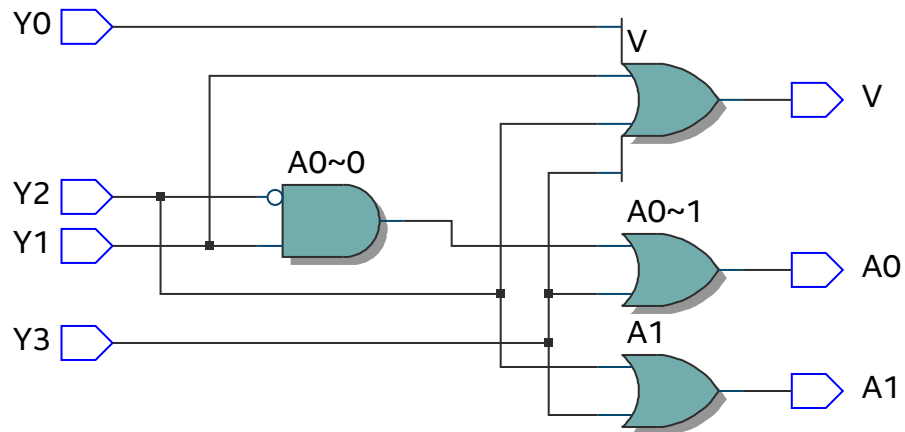

2. Write VHDL code to describe a truth table

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


a. Code

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY Exc2 IS
    PORT (
        X, Y, Z : IN STD_LOGIC;
        F : OUT STD_LOGIC
    );
END Exc2;
ARCHITECTURE Logic OF Exc2 IS
    SIGNAL input : std_logic_vector(2 DOWNTO 0);
BEGIN
    input(2) <= X;
    input(1) <= Y;
    input(0) <= Z;
    WITH input SELECT
    F <= '1' WHEN "001",
        '1' WHEN "110",
        '1' WHEN "111",
        '0' WHEN OTHERS;
END Logic;

```

b. Waveform

 

c. Result of RTL viewer

