

HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY – VNU HCMC
OFFICE FOR INTERNATIONAL STUDY PROGRAM
FACULTY OF ELECTRICAL AND ELECTRONIC ENGINEERING

————— * —————



DIGITAL SYSTEMS (LAB) EXPERIMENTAL REPORT (Lab 4)

Lecturer : **Mr. Nguyễn Tuấn Hùng**
Subject : **Digital Systems**
Class : **TT06**
Name : **Lương Triển Thắng**
Student ID : **2051194**

Ho Chi Minh City, 14th June, 2022

Contents

IV	Laboratory 4:	
	<i>Finite State Machines</i>	2
1.	Know how to implement a FSM circuit and download the circuit into the FPGA chip	2
a.	Code	2
b.	Waveform	4
c.	Result of RTL viewer	4
2.	Know how to implement a FSM circuit using VHDL behavioral expressions and download the circuit into the FPGA chip	6
a.	Code	6
b.	Waveform	7
c.	Result of RTL viewer	8
d.	State machine diagram and encoding types	8
3.	Know how to implement sequence detector using shift registers	9
a.	Code	9
b.	Waveform	10
c.	Result of RTL viewer	11
4.	Know how to implement a digital circuit using an FSM	12
a.	FSM diagram	12
b.	Code	12
c.	Waveform	15
d.	Result of RTL viewer	15
e.	State machine diagram	15

IV Laboratory 4

Finite State Machines

1. Know how to implement a FSM circuit and download the circuit into the FPGA chip

a. Code

DFFn.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY DFFn IS
    PORT (
        Din, DClk, Dprs, Dclr, Den : IN STD_LOGIC;
        DQ : OUT STD_LOGIC);
END DFFn;
ARCHITECTURE Behavior OF DFFn IS
BEGIN
    PROCESS (Dprs, Dclr, DClk)
    BEGIN
        IF Dclr = '1' AND Dprs = '0' THEN
            DQ <= '0';
        ELSIF Dclr = '0' AND Dprs = '1' THEN
            DQ <= '1';
        ELSE
            IF rising_edge(DClk) AND Den = '1' THEN
                DQ <= Din;
            END IF;
        END IF;
    END PROCESS;
END Behavior;
```

NineDFF.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY NineDFF IS
    PORT (
        NClk, Nen : IN STD_LOGIC;
        ND, Nprs, Nclr : IN STD_LOGIC_VECTOR(8 DOWNTO 0);
        NQ : OUT STD_LOGIC_VECTOR(8 DOWNTO 0)
    );
END NineDFF;

ARCHITECTURE arch OF NineDFF IS
    COMPONENT DFFn IS
        PORT (
            Din, DClk, Dprs, Dclr, Den : IN STD_LOGIC;
            DQ : OUT STD_LOGIC);
    END COMPONENT;
BEGIN
    gen : FOR i IN 8 DOWNTO 0 GENERATE
        DFFs : DFFn PORT MAP(
            Din => ND(i), DClk => NClk, Dprs => Nprs(i),
            Dclr => Nclr(i), Den => Nen, DQ => NQ(i));
    END GENERATE
END arch;
```

```

        END GENERATE;
END ARCHITECTURE;

```

Exc1.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY Exc1 IS
    PORT (
        clk, w, rstN : IN STD_LOGIC;
        LED : OUT STD_LOGIC_VECTOR(8 DOWNTO 0);
        z : OUT STD_LOGIC
    );
END Exc1;

ARCHITECTURE arch OF Exc1 IS
    SIGNAL D, Q, prsV, clrV : STD_LOGIC_VECTOR(8 DOWNTO 0);
    SIGNAL rst : STD_LOGIC;
    COMPONENT NineDFF IS
        PORT (
            NClk, Nen : IN STD_LOGIC;
            ND, Nprs, Nclr : IN STD_LOGIC_VECTOR(8 DOWNTO 0);
            NQ : OUT STD_LOGIC_VECTOR(8 DOWNTO 0)
        );
    END COMPONENT;
BEGIN
    rst <= NOT(rstN);

    D(8) <= w AND (Q(7) OR Q(8));
    D(7) <= Q(6) AND w;
    D(6) <= Q(5) AND w;
    D(5) <= w AND NOT(Q(5) OR Q(6) OR Q(7) OR Q(8));
    D(4) <= NOT(w) AND (Q(3) OR Q(4));
    D(3) <= Q(2) AND NOT(w);
    D(2) <= Q(1) AND NOT(w);
    D(1) <= NOT(Q(1) OR Q(2) OR Q(3) OR Q(4) OR w);
    D(0) <= '0';
    z <= Q(4) OR Q(8);

    -- FOR MODIFIED ONE-HOT
    --     D(8) <= w AND (Q(7) OR Q(8));
    --     D(7) <= Q(6) AND w;
    --     D(6) <= Q(5) AND w;
    --     D(5) <= w AND (NOT(Q(5) OR Q(6) OR Q(7) OR Q(8)));
    --     D(4) <= NOT(w) AND (Q(3) OR Q(4));
    --     D(3) <= Q(2) AND NOT(w);
    --     D(2) <= Q(1) AND NOT(w);
    --     D(1) <= NOT(Q(1) OR Q(2) OR Q(3) OR Q(4) OR w);
    --     D(0) <= '1';
    --     z <= Q(4) OR Q(8);

    LED <= Q;

    prsV <= "000000001" WHEN rst = '1' ELSE "000000000";
    clrV <= "111111110" WHEN rst = '1' ELSE "000000000";

    -- FOR MODIFIED ONE-HOT
    --     prsV <= "000000000" WHEN rst = '1' ELSE "000000000";
    --     clrV <= "111111111" WHEN rst = '1' ELSE "000000000";

    NDFF : NineDFF PORT MAP(

```


```

        NClk => clk, Nprs => prsV, Nclr => clrV,
        Nen => '1', ND => D, NQ => Q
    );
END ARCHITECTURE;


```

b. Waveform


One-hot

 


Modified one-hot

 


c. Result of RTL viewer

 


D flip-flop

 

Connected 9 D flip-flops

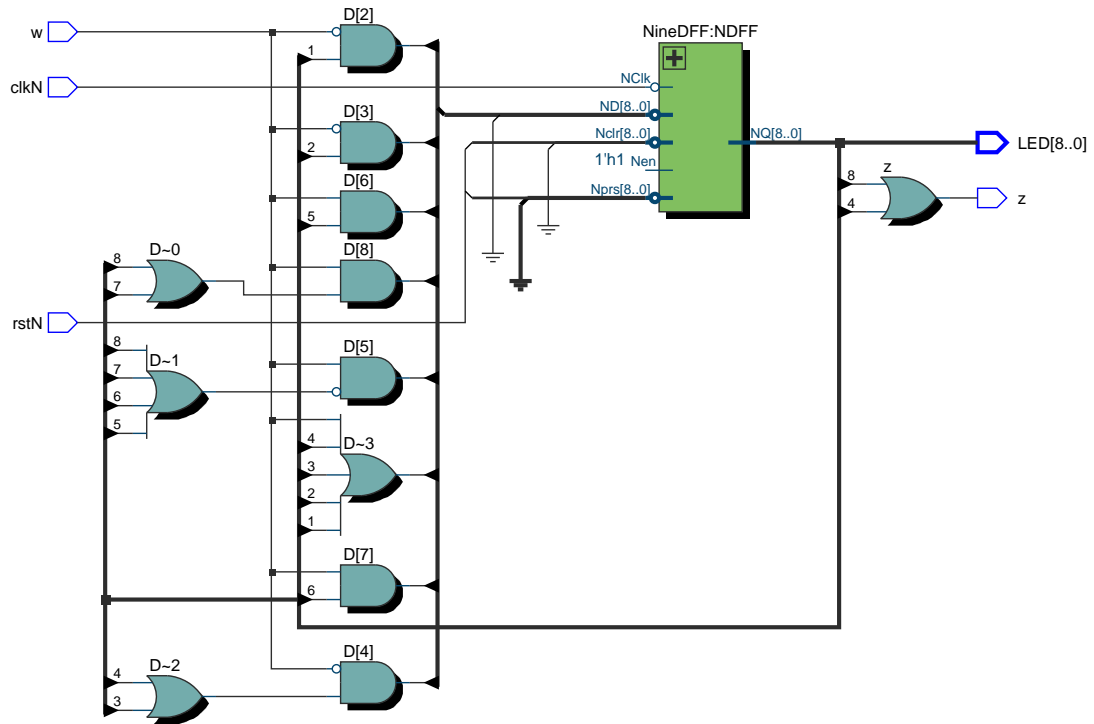

Top level (using one-hot encoding)

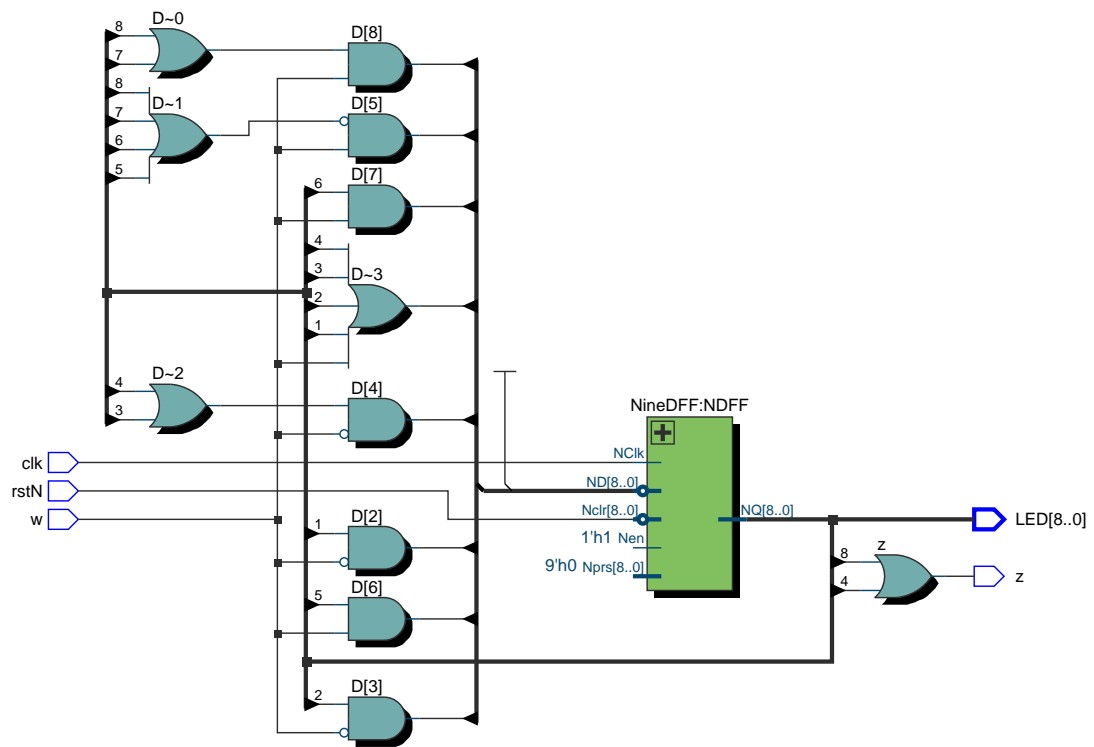

Top level (using modified one-hot encoding)

2. Know how to implement a FSM circuit using VHDL behavioral expressions and download the circuit into the FPGA chip

a. Code

Exc2.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY Exc2 IS PORT (
    w, clk, rst : IN STD_LOGIC;
    x : OUT STD_LOGIC
);
END Exc2;

ARCHITECTURE Behavior OF Exc2 IS
    TYPE State_type IS (A, B, C, D, E, F, G, H, I);
    ATTRIBUTE syn_encoding : STRING;
    ATTRIBUTE syn_encoding OF State_type : TYPE IS "0000 0001 0010 0011 0100 0101 0110 0111 1000";

    SIGNAL y_Q, Y_D : State_type;
BEGIN
    PROCESS (w, y_D)
    BEGIN
        CASE y_D IS
            WHEN A =>
                IF (w = '0') THEN
                    y_Q <= B;
                ELSE
                    y_Q <= F;
                END IF;

            WHEN B =>
                IF (w = '0') THEN
                    y_Q <= C;
                ELSE
                    y_Q <= F;
                END IF;

            WHEN C =>
                IF (w = '0') THEN
                    y_Q <= D;
                ELSE
                    y_Q <= F;
                END IF;

            WHEN D =>
                IF (w = '0') THEN
                    y_Q <= E;
                ELSE
                    y_Q <= F;
                END IF;

            WHEN E =>
                IF (w = '0') THEN
                    y_Q <= E;
                ELSE
                    y_Q <= F;
                END IF;

            -----
            WHEN F =>
```

```

        IF (w = '1') THEN
            y_Q <= G;
        ELSE
            y_Q <= B;
        END IF;

    WHEN G =>
        IF (w = '1') THEN
            y_Q <= H;
        ELSE
            y_Q <= B;
        END IF;

    WHEN H =>
        IF (w = '1') THEN
            y_Q <= I;
        ELSE
            y_Q <= B;
        END IF;


    WHEN I =>
        IF (w = '1') THEN
            y_Q <= I;
        ELSE
            y_Q <= B;
        END IF;

    END CASE;
END PROCESS;
x <= '1' WHEN y_D = E OR y_D = I ELSE '0';


PROCESS (clk, rst)
BEGIN
    IF rst = '1' THEN
        Y_D <= A;
    ELSE
        IF rising_edge(clk) THEN
            y_D <= y_Q;
        END IF;
    END IF;
END PROCESS;
END Behavior;

```

b. Waveform

 


c. Result of RTL viewer

 

Top level

 d. State machine diagram and encoding types



State machine diagram

	Name	Y_D~7	Y_D~6	Y_D~5	Y_D~4
1	Y_D.A	0	0	0	0
2	Y_D.B	0	0	0	1
3	Y_D.C	0	0	1	0
4	Y_D.D	0	0	1	1
5	Y_D.E	0	1	0	0
6	Y_D.F	0	1	0	1
7	Y_D.G	0	1	1	0
8	Y_D.H	0	1	1	1
9	Y_D.I	1	0	0	0
Encoding Type: User-Encoded					

	Name	Y_D.I	Y_D.H	Y_D.G	Y_D.F	Y_D.E	Y_D.D	Y_D.C	Y_D.B	Y_D.A
1	Y_D.A	0	0	0	0	0	0	0	0	0
2	Y_D.B	0	0	0	0	0	0	0	1	1
3	Y_D.C	0	0	0	0	0	0	1	0	1
4	Y_D.D	0	0	0	0	0	1	0	0	1
5	Y_D.E	0	0	0	0	1	0	0	0	1
6	Y_D.F	0	0	0	1	0	0	0	0	1
7	Y_D.G	0	0	1	0	0	0	0	0	1
8	Y_D.H	0	1	0	0	0	0	0	0	1
9	Y_D.I	1	0	0	0	0	0	0	0	1
Encoding Type: One-Hot										

Encoding types

3. Know how to implement sequence detector using shift registers

In this exercise, using two shift registers is a waste, so I will use only one shift register and connect it with some logic gates, that is enough.

a. Code

DFFn.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY DFFn IS
    PORT (
        Din, DClk, DprsN, DclrN, Den : IN STD_LOGIC; -- clr and prs are active low.
        DQ : OUT STD_LOGIC);
END DFFn;
ARCHITECTURE Behavior OF DFFn IS
BEGIN
    PROCESS (DprsN, DclrN, DClk)
    BEGIN
        IF DclrN = '0' AND DprsN = '1' THEN
            DQ <= '0';
        ELSIF DclrN = '1' AND DprsN = '0' THEN
            DQ <= '1';
        ELSE
            IF rising_edge(DClk) AND Den = '1' THEN
                DQ <= Din;
            END IF;
        END IF;
    END PROCESS;
END Behavior;
```

FourBitShiftReg.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY FourBitShiftReg IS
    PORT (
        SRegclk, SReginp, SRegrstN : IN STD_LOGIC;
        SRegL : OUT STD_LOGIC_VECTOR(0 TO 3)
    );
END FourBitShiftReg;

ARCHITECTURE arch OF FourBitShiftReg IS
    SIGNAL q : STD_LOGIC_VECTOR(0 TO 3) := "XXXX";
    COMPONENT DFFn IS
        PORT (
            Din, DClk, DprsN, DclrN, Den : IN STD_LOGIC;
            DQ : OUT STD_LOGIC);
    END COMPONENT;
BEGIN
    DFF0 : DFFn PORT MAP(
        Din => SReginp, DClk => SRegclk, DprsN => '1',
        DclrN => SRegrstN, Den => '1', DQ => q(0));
    gen : FOR i IN 1 TO 3 GENERATE
        DFFs : DFFn PORT MAP(
            Din => q(i - 1), DClk => SRegclk, DprsN => '1',
            DclrN => SRegrstN, Den => '1', DQ => q(i));
    END GENERATE;
END arch;
```

```

        SRegL <= q;
END ARCHITECTURE;

```

Exc2.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;


ENTITY Exc3 IS
    PORT (
        inp, clk, rstN : IN STD_LOGIC;
        z : OUT STD_LOGIC
    );
END Exc3;

ARCHITECTURE arch OF Exc3 IS
    SIGNAL L : STD_LOGIC_VECTOR(0 TO 3);
    SIGNAL waitFourClocks : UNSIGNED(2 DOWNT0 0) := "100";
    SIGNAL en : STD_LOGIC;
    COMPONENT FourBitShiftReg IS
        PORT (
            SRegclk, SReginp, SRegrstN : IN STD_LOGIC;
            SRegL : OUT STD_LOGIC_VECTOR(0 TO 3)
        );
    END COMPONENT;
BEGIN
    PROCESS (clk)
    BEGIN
        IF rstN = '0' THEN
            waitFourClocks <= "100";
        ELSIF rising_edge(clk) AND waitFourClocks /= 0 THEN
            waitFourClocks <= waitFourClocks - 1;
        END IF;
    END PROCESS;
    en <= '1' WHEN waitFourClocks = 0 ELSE '0';
    SR1 : FourBitShiftReg PORT MAP(SRegclk => clk, SReginp => inp, SRegrstN => rstN, SRegL => L);


    z <= '1' WHEN (L1 = "1111" OR L1 = "0000") AND en = '1' ELSE '0';
END ARCHITECTURE;

```


b. Waveform

 


c. Result of RTL viewer

 

D flip-flop

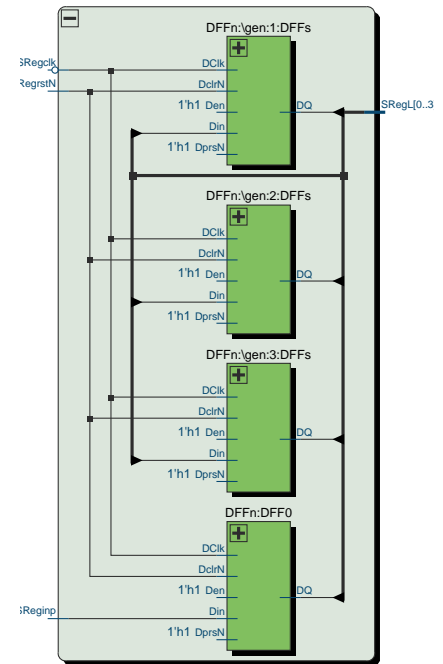

Four-bit shift register

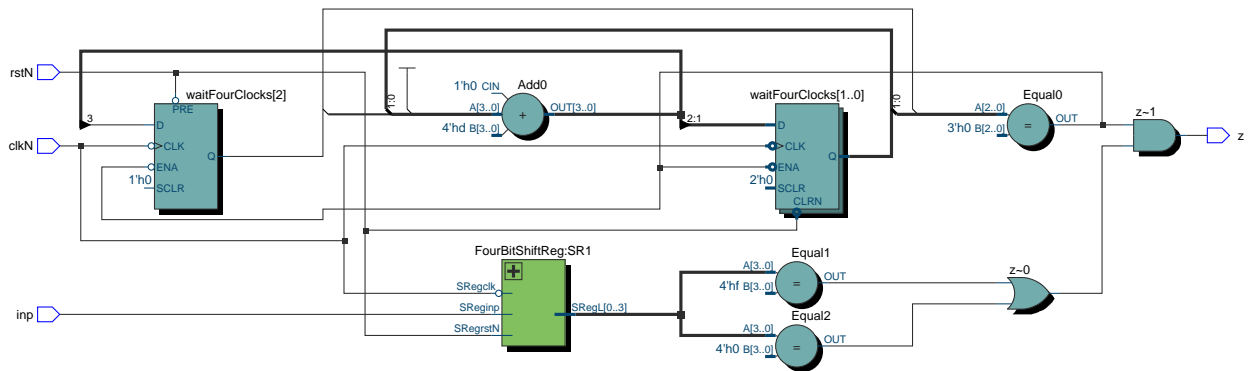


Top level

4. Know how to implement a digital circuit using an FSM

As I stated in PreLab 4, in this exercise, instead of using two LEDR and LEDG, I modified the circuit, so when there is a dot, LED will on for 0.25 second; when there is a dash, LED will on for 1 second.

a. FSM diagram

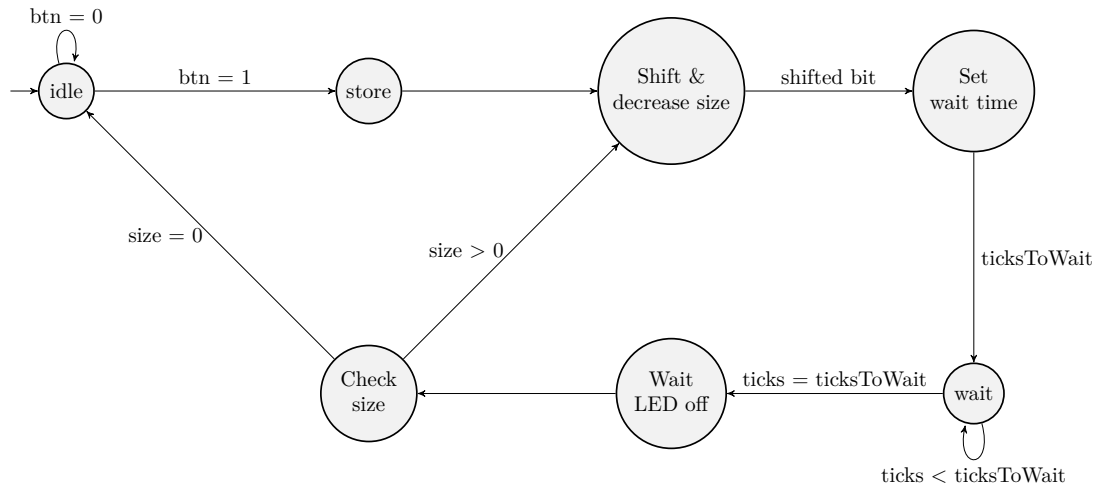

b. Code

Exc4.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY Exc4 IS
    PORT (
        letter : IN STD_LOGIC_VECTOR(2 DOWNTO 0);
        LED : OUT STD_LOGIC;
        clk, btnN, rstN : IN STD_LOGIC
    );
END Exc4;

ARCHITECTURE arch OF Exc4 IS
    SIGNAL morseCode : STD_LOGIC_VECTOR(3 DOWNTO 0);
    SIGNAL morseLength : STD_LOGIC_VECTOR(2 DOWNTO 0);
    SIGNAL bitIn, btn, rst : STD_LOGIC := '0';

    SIGNAL ticks, ticksToWait : INTEGER RANGE 0 TO 200 := 0; -- Change 200 to 50000000 if running on DE10.

    TYPE State_type IS (idle, store, shift, setWaitInterval, waitT, waitLEDOff, checkSize);
    SIGNAL state : State_type := idle;
    COMPONENT DFFn IS
        PORT (
            Din, DClk, Den : IN STD_LOGIC;
            DQ : OUT STD_LOGIC);
    END COMPONENT;

BEGIN
    btn <= NOT(btnN);
    rst <= NOT(rstN);
    PROCESS (clk, rst) IS
    BEGIN
```

```

IF rst = '1' THEN
    state <= idle;
ELSE
    IF rising_edge(clk) THEN
        CASE state IS
            WHEN idle =>
                LED <= '0';
                IF btn = '1' THEN
                    state <= store;
                ELSE
                    state <= idle;
                END IF;

            WHEN store =>
                CASE letter IS
                    WHEN "000" =>
                        morseCode <= "0010";
                        morseLength <= "010";
                    WHEN "001" =>
                        morseCode <= "0001";
                        morseLength <= "100";
                    WHEN "010" =>
                        morseCode <= "0101";
                        morseLength <= "100";
                    WHEN "011" =>
                        morseCode <= "0001";
                        morseLength <= "011";
                    WHEN "100" =>
                        morseCode <= "0000";
                        morseLength <= "001";
                    WHEN "101" =>
                        morseCode <= "0100";
                        morseLength <= "100";
                    WHEN "110" =>
                        morseCode <= "0011";
                        morseLength <= "011";
                    WHEN "111" =>
                        morseCode <= "0000";
                        morseLength <= "100";
                    WHEN OTHERS =>
                        morseCode <= "0000";
                        morseLength <= "000";
                END CASE;
                state <= shift;

            WHEN shift =>
                bitIn <= morseCode(0);
                morseCode <= '0' & morseCode(3 DOWNTO 1); -- Shift;
                morseLength <= STD_LOGIC_VECTOR(UNSIGNED(morseLength) - 1);
                state <= setWaitInterval;

            WHEN setWaitInterval =>
                -- clk at 200Hz
                -- ticksToWait = oldFreq / newFreq
                -- dot = 4Hz (0.25s), dash = 1Hz (1s)
                IF (bitIn = '0') THEN
                    ticksToWait <= 50; -- On DE10: 50MHz / 4Hz = 12500000
                ELSE
                    ticksToWait <= 200; -- On DE10: 50MHz / 1Hz = 50000000
                END IF;

                ticks <= 0; -- Reset ticks
                LED <= '1'; -- LED on

```

```

        state <= waitT;

    WHEN waitT =>
        IF ticks = ticksToWait - 1 THEN
            LED <= '0'; -- LED off
            ticks <= 0; -- Reset ticks
            state <= waitLEDOff;
            ticksToWait <= 100;
        ELSE
            ticks <= ticks + 1;
            state <= waitT;
        END IF;

    WHEN waitLEDOff =>
        IF ticks = ticksToWait - 1 THEN
            state <= checkSize;
            ticks <= 0; -- Reset ticks
        ELSE
            ticks <= ticks + 1;
            state <= waitLEDOff;
        END IF;

    WHEN checkSize =>
        IF morseLength = "000" THEN
            state <= idle;
        ELSE
            state <= shift;
        END IF;
    END CASE;
END IF;
END IF;
END PROCESS;
END ARCHITECTURE;

```

Exc4_tb.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY Exc4_tb IS
END ENTITY;

ARCHITECTURE sim OF Exc4_tb IS
    -- We're slowing down the clock to speed up simulation time
    CONSTANT ClockFrequencyHz : INTEGER := 200; -- 200 Hz
    CONSTANT ClockPeriod : TIME := 1000 ms / ClockFrequencyHz;

    SIGNAL letter : STD_LOGIC_VECTOR(2 DOWNTO 0) := "000";
    SIGNAL LED : STD_LOGIC;
    SIGNAL clk : STD_LOGIC := '1';
    SIGNAL btnN : STD_LOGIC := '0';
    SIGNAL rstN : STD_LOGIC := '1';

BEGIN
    -- The Device Under Test (DUT)
    morse : ENTITY work.Exc4(arch)
        PORT MAP(
            letter => letter,
            LED => LED,
            clk => clk,
            btnN => btnN,
            rstN => rstN
        );


```

```


-- Process for generating the clock
Clk <= NOT Clk AFTER ClockPeriod / 2;
PROCESS IS
BEGIN
    WAIT UNTIL rising_edge(clk);
    btnN <= '0';
    WAIT UNTIL rising_edge(clk);
    btnN <= '1';
    WAIT FOR 5000 ms;
    letter <= STD_LOGIC_VECTOR(UNSIGNED(letter) + 1);
END PROCESS;
END ARCHITECTURE;

```

c. Waveform

 

d. Result of RTL viewer

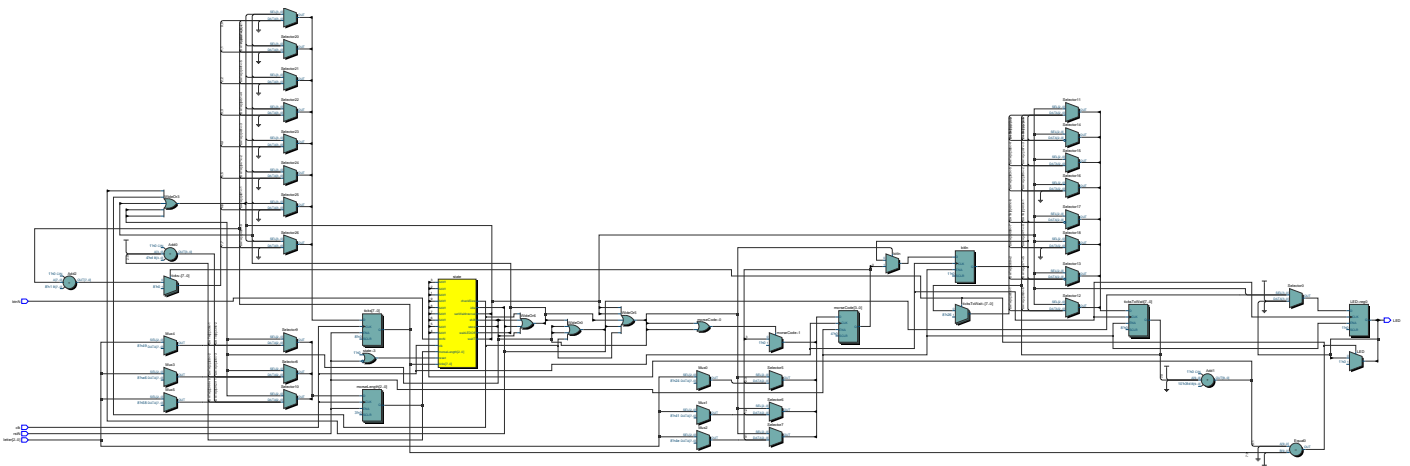

Top level (zoom in for better viewing)

e. State machine diagram

