

HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY – VNU HCMC
OFFICE FOR INTERNATIONAL STUDY PROGRAM
FACULTY OF ELECTRICAL AND ELECTRONIC ENGINEERING

————— * —————



DIGITAL SYSTEMS (LAB) EXPERIMENTAL REPORT (Lab 5)

Lecturer : **Mr. Nguyễn Tuấn Hùng**
Subject : **Digital Systems**
Class : **TT06**
Name : **Lương Triển Thắng**
Student ID : **2051194**

Ho Chi Minh City, 14th June, 2022

Contents

- V **Laboratory 5:**
 - A simple processor* **2**
 - 1. Design and implement a simple processor 2
 - a. Code 2
 - b. Waveform 7
 - c. Result of RTL viewer 8
 - 2. Design and implement a simple processor with memory 11
 - a. Code 11
 - b. Waveform 13
 - c. Result of RTL viewer 14

V Laboratory 5

A simple processor

1. Design and implement a simple processor

a. Code

DFF.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY DFFn IS
    PORT (
        D, clk, rst, en : IN STD_LOGIC;
        Q : OUT STD_LOGIC);
END DFFn;
ARCHITECTURE Behavior OF DFFn IS
BEGIN
    PROCESS (rst, clk, en)
    BEGIN
        IF rst = '1' THEN
            Q <= '0';
        ELSIF rising_edge(clk) AND en = '1' THEN
            Q <= D;
        END IF;
    END PROCESS;
END Behavior;
```

myReg.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY myReg IS
    PORT (
        clk, rst, en : IN STD_LOGIC;
        D : IN STD_LOGIC_VECTOR(8 DOWNTO 0);
        Q : OUT STD_LOGIC_VECTOR(8 DOWNTO 0)
    );
END myReg;

ARCHITECTURE arch OF myReg IS
    COMPONENT DFFn IS
        PORT (
            D, clk, rst, en : IN STD_LOGIC;
            Q : OUT STD_LOGIC);
    END COMPONENT;
BEGIN
    gen : FOR i IN 8 DOWNTO 0 GENERATE
        DFFs : DFFn PORT MAP(D(i), clk, rst, en, Q(i));
    END GENERATE;
END ARCHITECTURE;
```

RegMUX.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
```

```

ENTITY regMUX IS
    PORT (
        SIGNAL R0, R1, R2, R3, R4, R5, R6, R7 : IN STD_LOGIC_VECTOR(8 DOWNT0 0);
        SIGNAL g, DIN : IN STD_LOGIC_VECTOR(8 DOWNT0 0);
        SIGNAL sel : IN INTEGER RANGE 0 TO 10;
        SIGNAL MUXout : OUT STD_LOGIC_VECTOR(8 DOWNT0 0)
    );
END regMUX;

ARCHITECTURE arch OF regMUX IS
BEGIN
    WITH sel SELECT
        MUXout <=
            R0 WHEN 0,
            R1 WHEN 1,
            R2 WHEN 2,
            R3 WHEN 3,
            R4 WHEN 4,
            R5 WHEN 5,
            R6 WHEN 6,
            R7 WHEN 7,
            g WHEN 8,
            DIN WHEN 9,
            "00000000" WHEN 10;
END ARCHITECTURE;

```

AddSub.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY AddSub IS
    PORT (
        SIGNAL A, B : IN STD_LOGIC_VECTOR(8 DOWNT0 0);
        SIGNAL sel : IN STD_LOGIC;
        SIGNAL C : OUT STD_LOGIC_VECTOR(8 DOWNT0 0)
    );
END AddSub;

ARCHITECTURE arch OF AddSub IS
BEGIN
    C <= STD_LOGIC_VECTOR(UNSIGNED(A) + UNSIGNED(B)) WHEN sel = '0' ELSE
        STD_LOGIC_VECTOR(UNSIGNED(A) - UNSIGNED(B));
END ARCHITECTURE;

```

ctrlunitFSM.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY ctrlunitFSM IS
    PORT (
        SIGNAL rin : OUT STD_LOGIC_VECTOR(0 TO 7);
        SIGNAL ain, gin, IRin, addsub : OUT STD_LOGIC;
        SIGNAL IR : IN STD_LOGIC_VECTOR(8 DOWNT0 0);
        SIGNAL outsel : OUT INTEGER RANGE 0 TO 10;
        SIGNAL run, rst, clk : IN STD_LOGIC;
        SIGNAL done : BUFFER STD_LOGIC
    );
END ctrlunitFSM;

```

```

ARCHITECTURE arch OF ctrlunitFSM IS
    TYPE State_type IS (T0, T1, T2, T3);
    SIGNAL Tstep_Q, Tstep_D : State_type;

    SIGNAL opcode : STD_LOGIC_VECTOR(2 DOWNTO 0);
    SIGNAL RX, RY : NATURAL RANGE 0 TO 7;

BEGIN
    opcode <= IR(8 DOWNTO 6);
    RX <= TO_INTEGER(UNSIGNED(IR(5 DOWNTO 3)));
    RY <= TO_INTEGER(UNSIGNED(IR(2 DOWNTO 0)));
    statetable :
    PROCESS (Tstep_D, run)
    BEGIN
        CASE Tstep_D IS
            WHEN T0 =>
                IF run = '0' THEN
                    Tstep_Q <= T0;
                ELSE
                    Tstep_Q <= T1;
                END IF;
                -- data IS loaded into IR IN this TIME step
            WHEN T1 =>
                IF done = '1' THEN
                    Tstep_Q <= T0;
                ELSE
                    Tstep_Q <= T2;
                END IF;
            WHEN T2 =>
                Tstep_Q <= T3;
            WHEN T3 =>
                IF done = '1' THEN
                    Tstep_Q <= T0;
                ELSE
                    -- ERROR
                END IF;
            WHEN OTHERS => NULL;
        END CASE;
    END PROCESS;

    controlsignals :
    PROCESS (Tstep_D, IR, opcode, RX, RY)
    BEGIN
        rin <= (OTHERS => '0');
        ain <= '0';
        gin <= '0';
        outsel <= 10;
        addsub <= '0';
        CASE Tstep_D IS
            WHEN T0 => -- store DIN IN IR as long as Tstep_Q = 0
                IRin <= '1';
                done <= '0';
                outsel <= 9;
            WHEN T1 =>
                CASE opcode IS
                    WHEN "000" =>
                        outsel <= RY;
                        done <= '1';
                        rin(RX) <= '1';
                    WHEN "001" =>
                        outsel <= 9;
                        done <= '1';
                        rin(RX) <= '1';
                END CASE;
            -- Other cases for T2 and T3 would follow a similar pattern
        END CASE;
    END PROCESS;
END ARCHITECTURE arch;

```

```

        WHEN "010" | "011" =>
            outsel <= RX;
            ain <= '1';
        WHEN OTHERS => NULL;
    END CASE;
WHEN T2 =>
    CASE opcode IS
        WHEN "010" =>
            outsel <= RY;
            gin <= '1';
        WHEN "011" =>
            outsel <= RY;
            gin <= '1';
            addsub <= '1';
        WHEN OTHERS => NULL;
    END CASE;
WHEN T3 =>
    CASE opcode IS
        WHEN "010" | "011" =>
            outsel <= 8;
            rin(RX) <= '1';
            done <= '1';
        WHEN OTHERS => NULL;
    END CASE;
    WHEN OTHERS => NULL;
END CASE;
END PROCESS;
flipflops : PROCESS (clk, rst, Tstep_Q)
BEGIN
    IF rst = '1' THEN
        Tstep_D <= T0;
    ELSIF rising_edge(clk) THEN
        Tstep_D <= Tstep_Q;
    END IF;
END PROCESS;
END ARCHITECTURE;

```

Exc1.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY Exc1 IS
    PORT (
        R0out, R1out, Aout, Gout, IRout : OUT STD_LOGIC_VECTOR(8 DOWNTO 0);
        DIN : IN STD_LOGIC_VECTOR(8 DOWNTO 0);
        rstN, clk, run : IN STD_LOGIC;
        done : BUFFER STD_LOGIC;
        BusWires : BUFFER STD_LOGIC_VECTOR(8 DOWNTO 0)
    );
END Exc1;

ARCHITECTURE Behavior OF Exc1 IS
    -- MISC
    SIGNAL addOrSub : STD_LOGIC;

    -- REGISTERS, A, G, IR
    SIGNAL regin : STD_LOGIC_VECTOR(0 TO 7);
    SIGNAL A, G, Gt : STD_LOGIC_VECTOR(8 DOWNTO 0);
    SIGNAL ain, gin, IRin, rst : STD_LOGIC;
    SIGNAL R0, R1, R2, R3, R4, R5, R6, R7, IR : STD_LOGIC_VECTOR(8 DOWNTO 0);
    SIGNAL sel : INTEGER RANGE 0 TO 10;

```

```

COMPONENT myReg IS
    PORT (
        clk, rst, en : IN STD_LOGIC;
        D : IN STD_LOGIC_VECTOR(8 DOWNTO 0);
        Q : OUT STD_LOGIC_VECTOR(8 DOWNTO 0)
    );
END COMPONENT;

COMPONENT AddSub IS
    PORT (
        SIGNAL A, B : IN STD_LOGIC_VECTOR(8 DOWNTO 0);
        SIGNAL sel : IN STD_LOGIC;
        SIGNAL C : OUT STD_LOGIC_VECTOR(8 DOWNTO 0)
    );
END COMPONENT;

BEGIN

    R0out <= R0;
    R1out <= R1;
    Aout <= A;
    Gout <= G;
    IRout <= IR;

    rst <= NOT(rstN);
    -- ADDSUB
    as : AddSub PORT MAP(A, BusWires, addOrSub, Gt);

    -- REGS
    reg0 : myReg PORT MAP(clk, rst, regin(0), BusWires, R0);
    reg1 : myReg PORT MAP(clk, rst, regin(1), BusWires, R1);
    reg2 : myReg PORT MAP(clk, rst, regin(2), BusWires, R2);
    reg3 : myReg PORT MAP(clk, rst, regin(3), BusWires, R3);
    reg4 : myReg PORT MAP(clk, rst, regin(4), BusWires, R4);
    reg5 : myReg PORT MAP(clk, rst, regin(5), BusWires, R5);
    reg6 : myReg PORT MAP(clk, rst, regin(6), BusWires, R6);
    reg7 : myReg PORT MAP(clk, rst, regin(7), BusWires, R7);
    Areg : myReg PORT MAP(clk, rst, ain, BusWires, A);
    Greg : myReg PORT MAP(clk, rst, Gin, Gt, G);
    IRreg : myReg PORT MAP(clk, rst, IRin, DIN, IR);


    -- MUX
    regMUX0 : ENTITY work.RegMUX PORT MAP(R0, R1, R2, R3, R4, R5, R6, R7, G, DIN, sel, BusWires);

    -- FSM
    ControlUnit : ENTITY work.ctrlUnitFSM PORT MAP(
        regin, ain, gin, IRin, addorsub, IR, sel, run, rst, clk, done
    );


END ARCHITECTURE;

```

b. Waveform

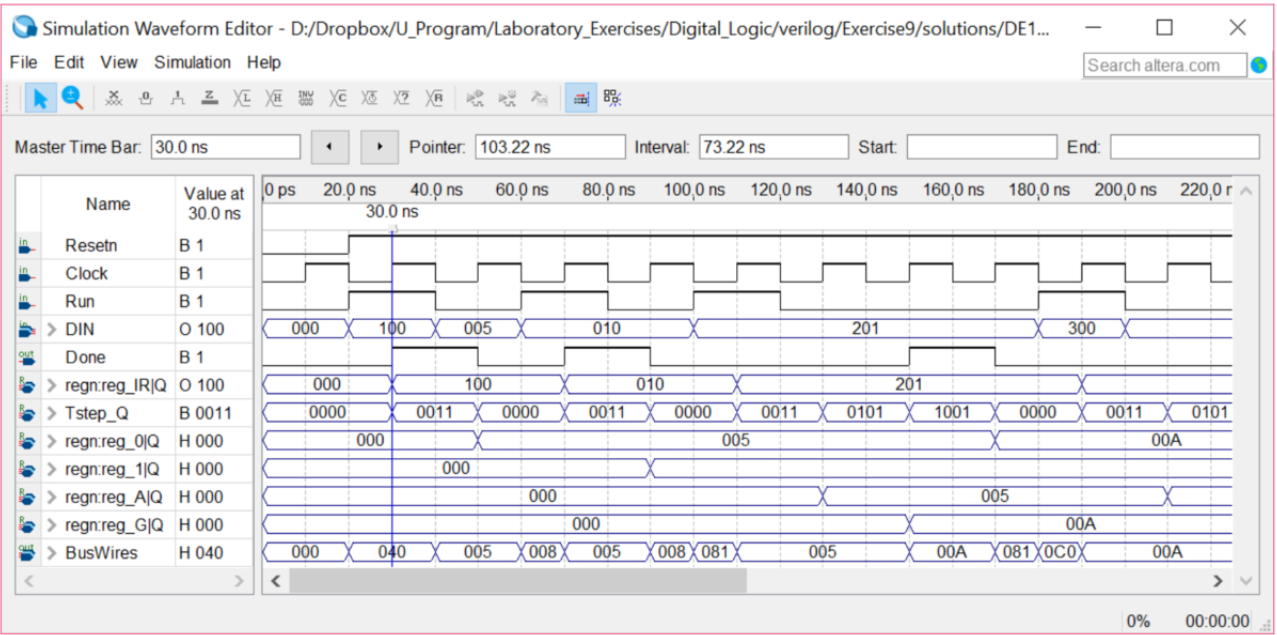



Reference waveform

 


Simulation result

c. Result of RTL viewer

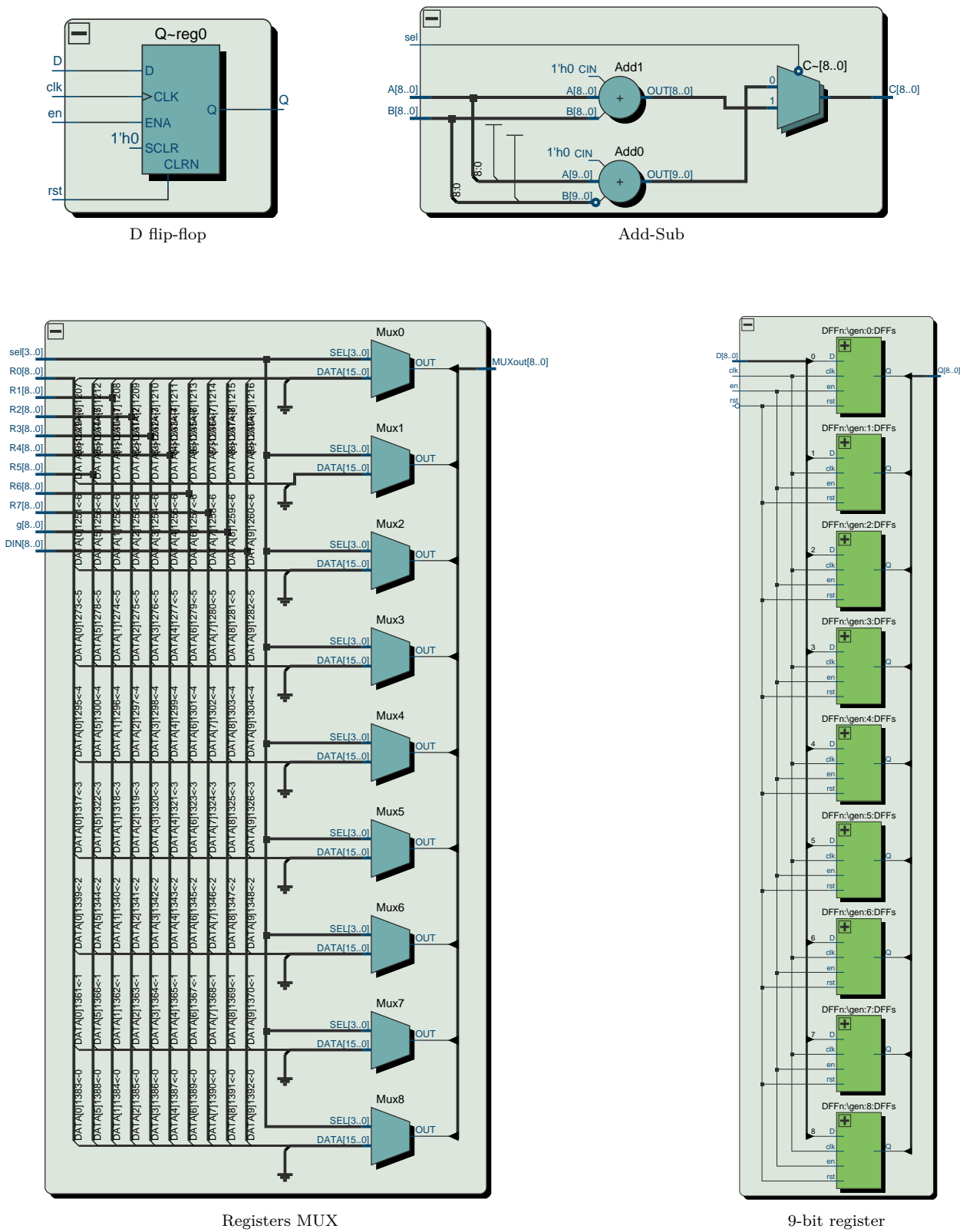

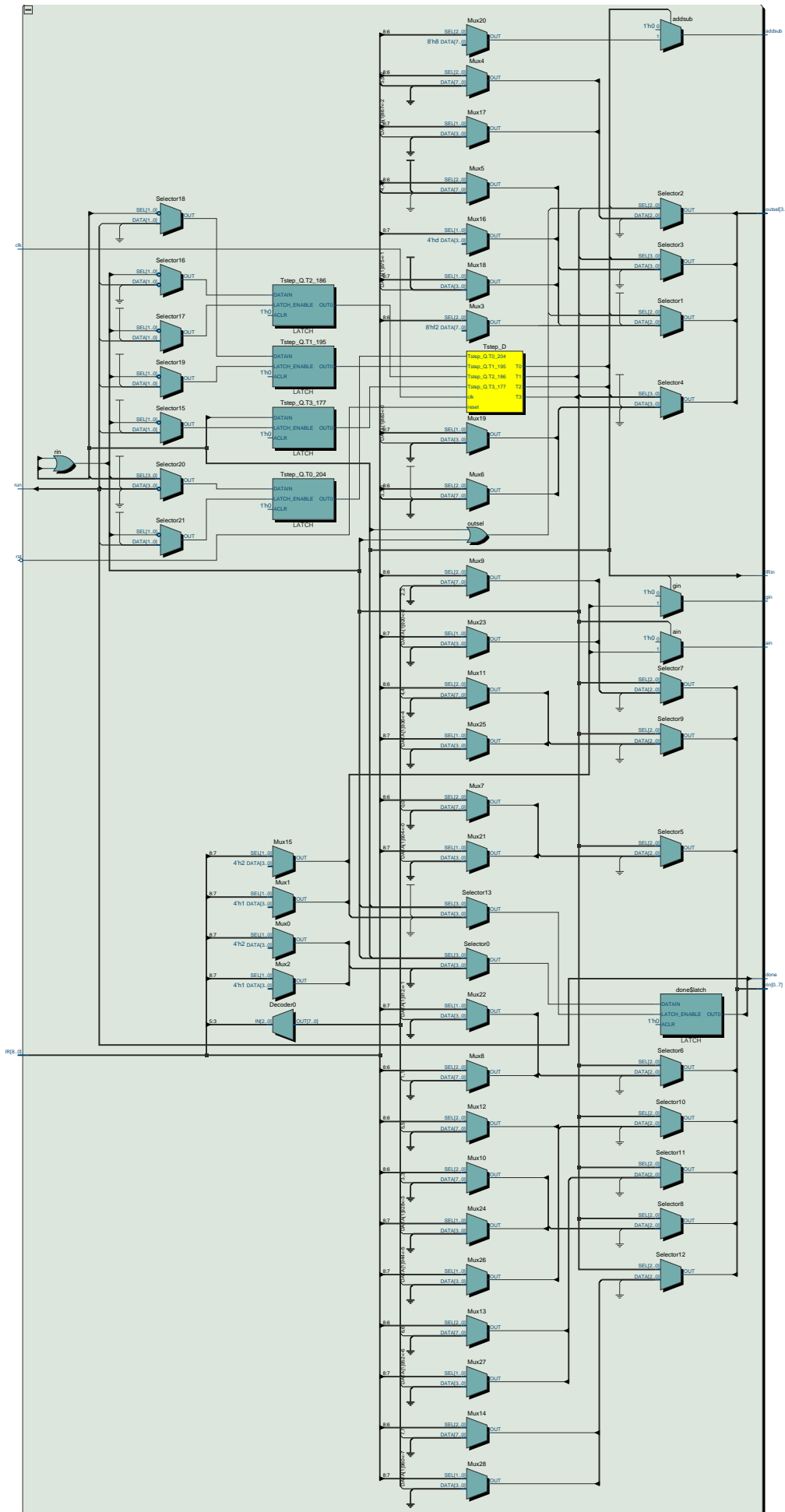

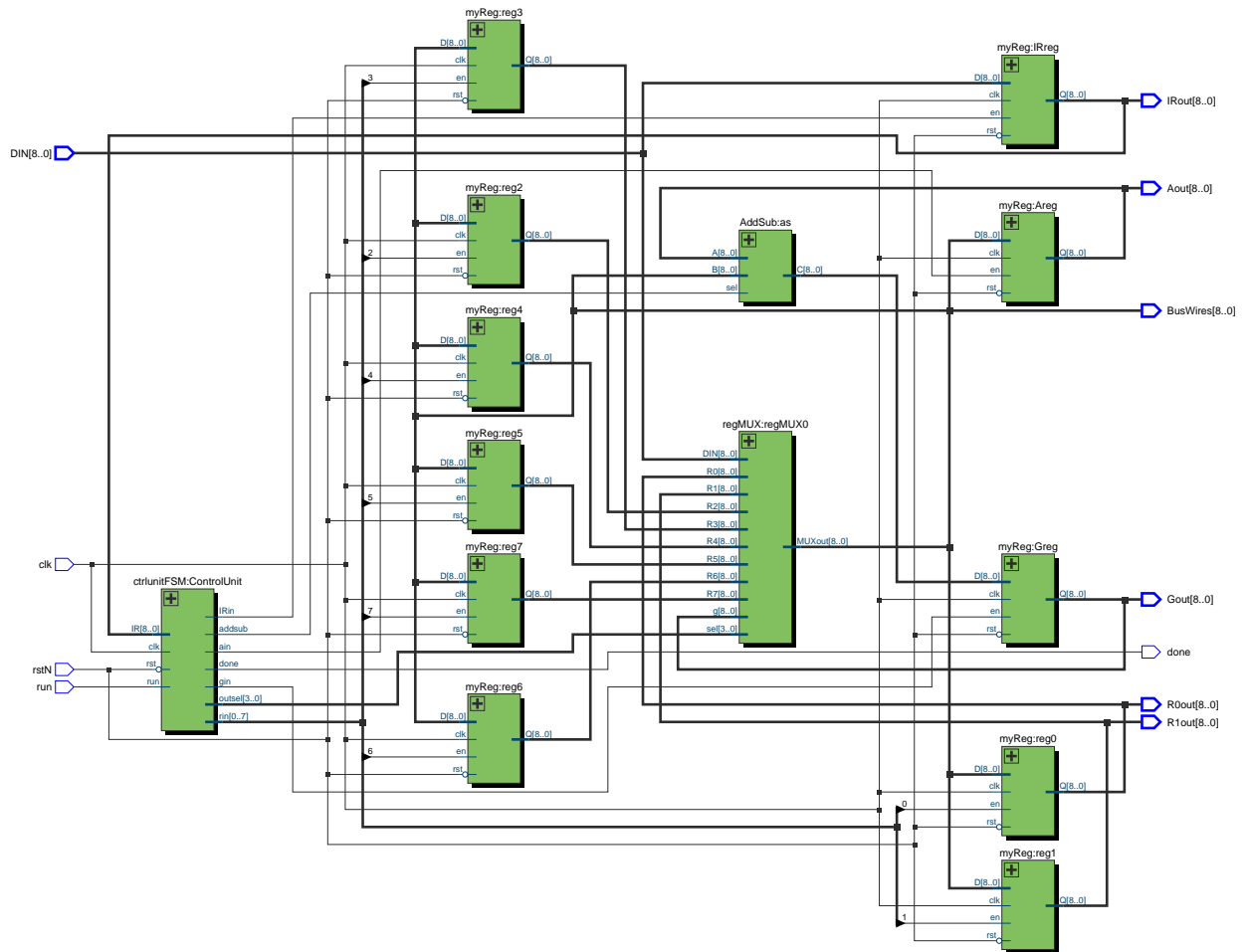Control Unit (zoom in for better viewing)



Top level (zoom in for better viewing)

2. Design and implement a simple processor with memory

This exercise is just an extension of the previous, so I just propose the additional parts.

I will change the circuit, so that 'run' will be not required to set manually in waveform, but in the ROM itself instead. A ROM data now contains 10 bits with MSB is 'run'. See the code section for the ROM and waveform to learn more.

A better version of this processor will be introduced in the report of Lab6.

a. Code

myROM.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY myROM IS
    GENERIC (
        addr_width : INTEGER := 32; -- store 32 elements
        addr_bits   : INTEGER := 5;  -- required bits to store 32 elements
        data_width  : INTEGER := 10 -- each element has 10-bits
    );
    PORT (
        addr : IN STD_LOGIC_VECTOR(addr_bits - 1 DOWNTO 0);
        data, nextData : OUT STD_LOGIC_VECTOR(data_width - 1 DOWNTO 0)
    );
END myROM;

ARCHITECTURE arch OF myROM IS
    TYPE rom_type IS ARRAY (0 TO addr_width - 1) OF STD_LOGIC_VECTOR(data_width - 1 DOWNTO 0);
    SIGNAL user_ROM : rom_type;
    SIGNAL address : INTEGER RANGE 0 TO addr_width - 1;

    ATTRIBUTE ram_init_file : STRING;
    ATTRIBUTE ram_init_file OF user_ROM : SIGNAL IS "rom_data.mif";

BEGIN
    address <= to_integer(unsigned(addr));
    data <= user_ROM (address);
    nextData <= user_ROM (address + 1);
END arch;
```

rom_data.mif

```
WIDTH=10;
DEPTH=32;

ADDRESS_RADIX=UNS;
DATA_RADIX=BIN;

CONTENT BEGIN
    [0..31] : 0000000000;
    0 : 0000000000;
    1 : 1001000000;
    2 : 0000000101;
    3 : 1000001000;
    4 : 1010000001;
    5 : 1011000000;
    6 : 1000000001;
END;
```

Exc2.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY Exc2 IS
    PORT (
        clk, rstN : IN STD_LOGIC;
        run, done : BUFFER STD_LOGIC;
        addrout : OUT STD_LOGIC_VECTOR(4 DOWNTO 0);
        dataOut : OUT STD_LOGIC_VECTOR(9 DOWNTO 0);
        ROout, RIout, Aout, Gout, IRout : OUT STD_LOGIC_VECTOR(8 DOWNTO 0);
        busWires : OUT STD_LOGIC_VECTOR(8 DOWNTO 0)
    );
END Exc2;

ARCHITECTURE arch OF Exc2 IS
    -- signal to store received data
    SIGNAL data, nextData : STD_LOGIC_VECTOR (9 DOWNTO 0);
    SIGNAL IR : STD_LOGIC_VECTOR(8 DOWNTO 0);
    SIGNAL addr : STD_LOGIC_VECTOR(4 DOWNTO 0) := "00000";
    SIGNAL mclk, isIR : STD_LOGIC;

    TYPE states IS (T0, T1, T2);
    SIGNAL state : states;

    COMPONENT Exc1 IS
        PORT (
            ROout, RIout, Aout, Gout, IRout : OUT STD_LOGIC_VECTOR(8 DOWNTO 0);
            DIN : IN STD_LOGIC_VECTOR(8 DOWNTO 0);
            rstN, clk, run : IN STD_LOGIC;
            done : BUFFER STD_LOGIC;
            BusWires : BUFFER STD_LOGIC_VECTOR(8 DOWNTO 0)
        );
    END COMPONENT;
BEGIN
    user_ROM : ENTITY work.myROM PORT MAP (addr, data, nextData);

    processor : Exc1 PORT MAP(ROout, RIout, Aout, Gout, IRout, IR, rstN, clk, run, done, busWires);

    run <= data(9);
    IR <= data(8 DOWNTO 0);

    addrout <= addr;
    dataOut <= data;


    PROCESS (clk, rstN, done)
    BEGIN
        IF rstN = '0' THEN
            state <= T0;
            addr <= "00000";
        ELSIF falling_edge(clk) THEN
            CASE state IS
                WHEN T0 =>
                    addr <= STD_LOGIC_VECTOR(UNSIGNED(addr) + 1);
                    state <= T1;
                WHEN T1 =>
                    IF done = '1' THEN
                        IF nextData(9) = '0' THEN
                            addr <= STD_LOGIC_VECTOR(UNSIGNED(addr) + 1);
                        END IF;
                        state <= T0;
                    END IF;
                END CASE;
            END PROCESS;
END arch;
```

```


ELSE
    state <= T1;
END IF;
WHEN T2 => NULL;
END CASE;
END IF;
END PROCESS;
END arch;

```

b. Waveform

 


Simulation result of Exc1

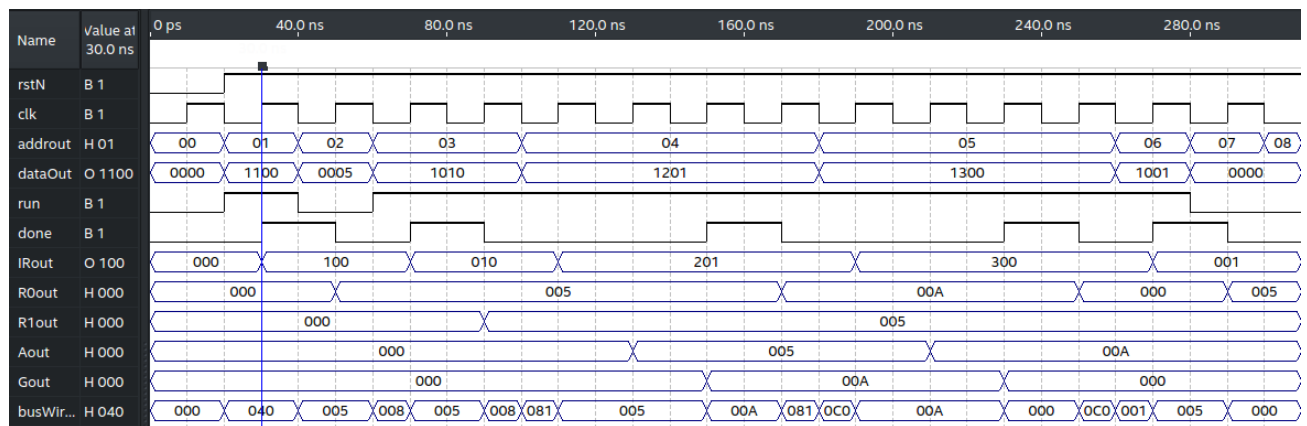


Simulation result

c. Result of RTL viewer

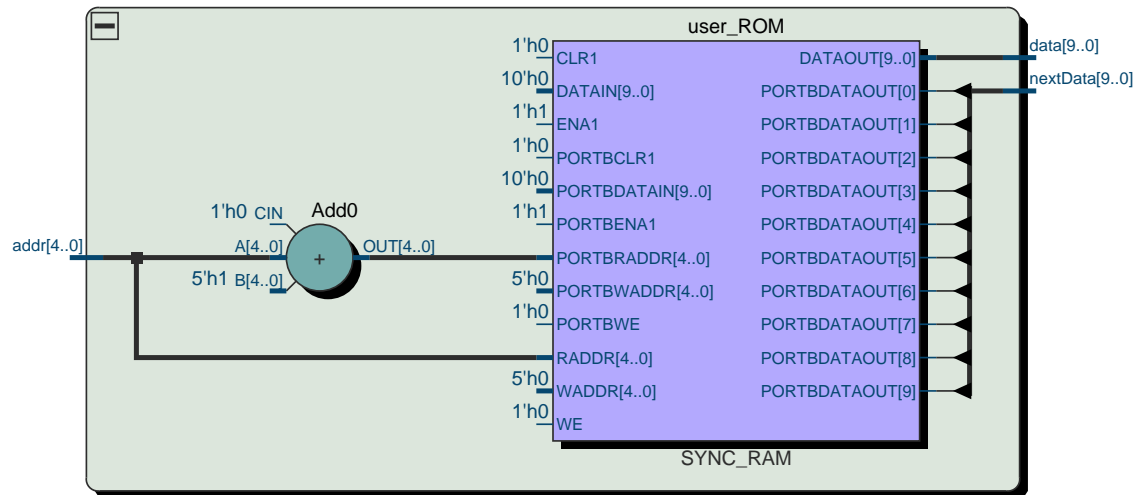

Read-only memory (ROM)

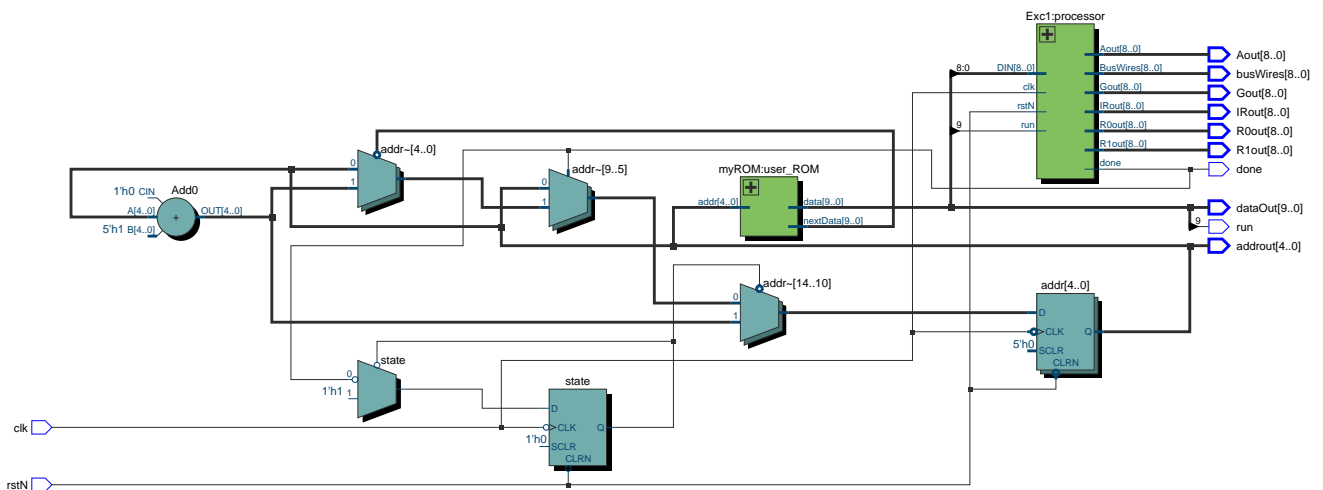

Top level (zoom in for better viewing)