

HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY – VNU HCMC
OFFICE FOR INTERNATIONAL STUDY PROGRAM
FACULTY OF ELECTRICAL AND ELECTRONIC ENGINEERING

————— * —————



DIGITAL SYSTEMS (LAB) EXPERIMENTAL REPORT (PreLab 4)

Lecturer : **Mr. Nguyễn Tuấn Hùng**
Subject : **Digital Systems**
Class : **TT06**
Name : **Lương Triển Thắng**
Student ID : **2051194**

Ho Chi Minh City, 7th June, 2022

Contents

IV	Pre Laboratory 4:	
	<i>Finite State Machines</i>	2
1.	Create state diagram and build the circuit for a finite state machine . . .	2
a.	Next state table	2
b.	Functions for flip-flops	2
c.	Circuit diagram	2
2.	Describe FSM using VHDL behavioral expressions	3
3.	Implement a shift register	4
a.	Code	4
b.	Waveform	5
c.	Result of RTL viewer	5
4.	Implement a periodic signal	6
a.	Code	6
b.	Waveform	7
c.	Result of RTL viewer	7
5.	Know how to implement a digital circuit using an FSM	7
a.	FSM diagram	7
b.	Details	8
c.	Expected waveform	8

IV Pre Laboratory 4

Finite State Machines

1. Create state diagram and build the circuit for a finite state machine


a. Next state table

Present State		Next State				Output	
		$w = 0$		$w = 1$		$w = 0$	$w = 1$
<i>A</i>	000000001	<i>B</i>	000000010	<i>F</i>	000100000	0	0
<i>B</i>	000000010	<i>C</i>	000000100	<i>F</i>	000100000	0	0
<i>C</i>	000000100	<i>D</i>	000001000	<i>F</i>	000100000	0	0
<i>D</i>	000001000	<i>E</i>	000010000	<i>F</i>	000100000	0	0
<i>E</i>	000010000	<i>E</i>	000010000	<i>F</i>	000100000	1	0
<i>F</i>	000100000	<i>B</i>	000000010	<i>G</i>	001000000	0	0
<i>G</i>	001000000	<i>B</i>	000000010	<i>H</i>	010000000	0	0
<i>H</i>	010000000	<i>B</i>	000000010	<i>I</i>	100000000	0	0
<i>I</i>	100000000	<i>B</i>	000000010	<i>I</i>	100000000	0	1
Others	×	Others	×	Others	×	×	×

b. Functions for flip-flops

$$\begin{aligned}
 D_8 &= w(Q_7 + Q_8) & D_5 &= \overline{Q_5}\overline{Q_6}\overline{Q_7}\overline{Q_8}w & D_2 &= Q_1\overline{w} \\
 D_7 &= Q_6w & D_4 &= \overline{w}(Q_3 + Q_4) & D_1 &= \overline{Q_1}\overline{Q_2}\overline{Q_3}\overline{Q_4}\overline{w} \\
 D_6 &= Q_5w & D_3 &= Q_2\overline{w} & z &= \overline{Q_4} + \overline{Q_8}
 \end{aligned}$$

c. Circuit diagram

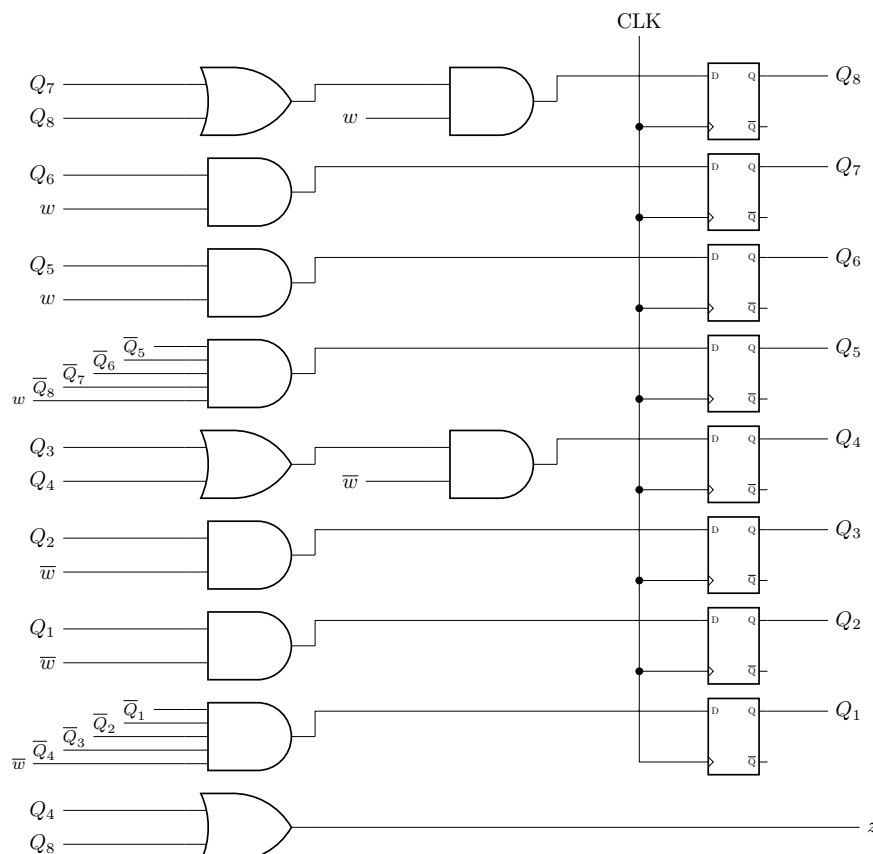

2. Describe FSM using VHDL behavioral expressions

Exc2.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY Exc2 IS PORT (
    w, clk, rst : IN STD_LOGIC;
    x : OUT STD_LOGIC
);
END Exc2;

ARCHITECTURE Behavior OF Exc2 IS
    TYPE State_type IS (A, B, C, D, E, F, G, H, I);
    ATTRIBUTE syn_encoding : STRING;
    ATTRIBUTE syn_encoding OF State_type : TYPE IS "0000 0001 0010 0011 0100 0101 0110 0111 1000";

    SIGNAL y_Q, Y_D : State_type;
BEGIN
    PROCESS (w, y_D)
    BEGIN
        CASE y_D IS
            WHEN A =>
                IF (w = '0') THEN
                    y_Q <= B;
                ELSE
                    y_Q <= F;
                END IF;

            WHEN B =>
                IF (w = '0') THEN
                    y_Q <= C;
                ELSE
                    y_Q <= F;
                END IF;

            WHEN C =>
                IF (w = '0') THEN
                    y_Q <= D;
                ELSE
                    y_Q <= F;
                END IF;

            WHEN D =>
                IF (w = '0') THEN
                    y_Q <= E;
                ELSE
                    y_Q <= F;
                END IF;

            WHEN E =>
                IF (w = '0') THEN
                    y_Q <= E;
                ELSE
                    y_Q <= F;
                END IF;

            -----
            WHEN F =>
                IF (w = '1') THEN
                    y_Q <= G;
                ELSE
                    y_Q <= B;
                END IF;
        END CASE;
    END PROCESS;
END Behavior;
```

```

        END IF;

    WHEN G =>
        IF (w = '1') THEN
            y_Q <= H;
        ELSE
            y_Q <= B;
        END IF;

    WHEN H =>
        IF (w = '1') THEN
            y_Q <= I;
        ELSE
            y_Q <= B;
        END IF;

    WHEN I =>
        IF (w = '1') THEN
            y_Q <= I;
        ELSE
            y_Q <= B;
        END IF;

    END CASE;
END PROCESS;
x <= '1' WHEN y_D = E OR y_D = I ELSE '0';

PROCESS (clk, rst)
BEGIN
    IF rst = '1' THEN
        Y_D <= A;
    ELSE
        IF rising_edge(clk) THEN
            y_D <= y_Q;
        END IF;
    END IF;
END PROCESS;
END Behavior;

```

3. Implement a shift register

a. Code

Exc3.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY Exc3 IS
    PORT (
        clk, inp, rst : IN STD_LOGIC;    -- rst: active low
        L : OUT STD_LOGIC_VECTOR(0 TO 3)
    );
END Exc3;

ARCHITECTURE arch OF Exc3 IS
    SIGNAL q : STD_LOGIC_VECTOR(0 TO 3);
    COMPONENT DFFn IS
        PORT (
            Din, DClk, DprsN, DclrN, Den : IN STD_LOGIC; -- clr and prs are active low.
            DQ : OUT STD_LOGIC);
    END COMPONENT;


```

```


BEGIN
  DFF0 : DFFn PORT MAP(
    Din => inp, DClk => clk, DprsN => '1',
    DclrN => rst, Den => '1', DQ => q(0));
  gen : FOR i IN 1 TO 3 GENERATE
    DFFs : DFFn PORT MAP(
      Din => q(i - 1), DClk => clk, DprsN => '1',
      DclrN => rst, Den => '1', DQ => q(i));
  END GENERATE;
  L <= q;
END ARCHITECTURE;

```

b. Waveform

 

c. Result of RTL viewer

 

4. Implement a periodic signal

a. Code

Exc4.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY Exc4 IS
    GENERIC (rate : INTEGER); -- rate = oldFreq / newFreq
    PORT (
        Clk : IN STD_LOGIC;
        clkout : OUT STD_LOGIC;
        nRst : IN STD_LOGIC -- Negative reset
    );
END ENTITY;

ARCHITECTURE rtl OF Exc4 IS
    -- Signal for counting clock periods
    SIGNAL Ticks : INTEGER := 0;
    SIGNAL clkt : STD_LOGIC := '0';

BEGIN
    clkout <= clkt;
    PROCESS (Clk) IS
    BEGIN
        IF rising_edge(Clk) THEN
            -- If the negative reset signal is active
            IF nRst = '0' THEN
                Ticks <= 0;
            ELSE
                IF Ticks = (rate / 2) - 1 THEN
                    Ticks <= 0;
                    clkt <= NOT (clkt);
                ELSE
                    Ticks <= Ticks + 1;
                END IF;
            END IF;
        END IF;
    END PROCESS;
END ARCHITECTURE;
```

Exc4_tb.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY Exc4_tb IS
END ENTITY;

ARCHITECTURE sim OF Exc4_tb IS

    -- We're slowing down the clock to speed up simulation time
    CONSTANT ClockFrequencyHz : INTEGER := 10; -- 10 Hz; 50 MHz or 25 MHz for the clock on DE10
    CONSTANT ClockPeriod : TIME := 1000 ms / ClockFrequencyHz;

    SIGNAL Clk : STD_LOGIC := '1';
    SIGNAL nRst : STD_LOGIC := '1';
    SIGNAL clkout : STD_LOGIC;
```


BEGIN

```
-- The Device Under Test (DUT)
CD : ENTITY work.Exc4(rtl)
  GENERIC MAP(rate => 10)
  PORT MAP(
    Clk => Clk,
    nRst => nRst,
    clkout => clkout);


-- Process for generating the clock
Clk <= NOT Clk AFTER ClockPeriod / 2;
```

END ARCHITECTURE;

b. Waveform

 


c. Result of RTL viewer

 

5. Know how to implement a digital circuit using an FSM

In this exercise, I modified the circuit, so when there is a dot, LED will on for 0.25 second; if there is a dash, LED will on for 1 second.

a. FSM diagram

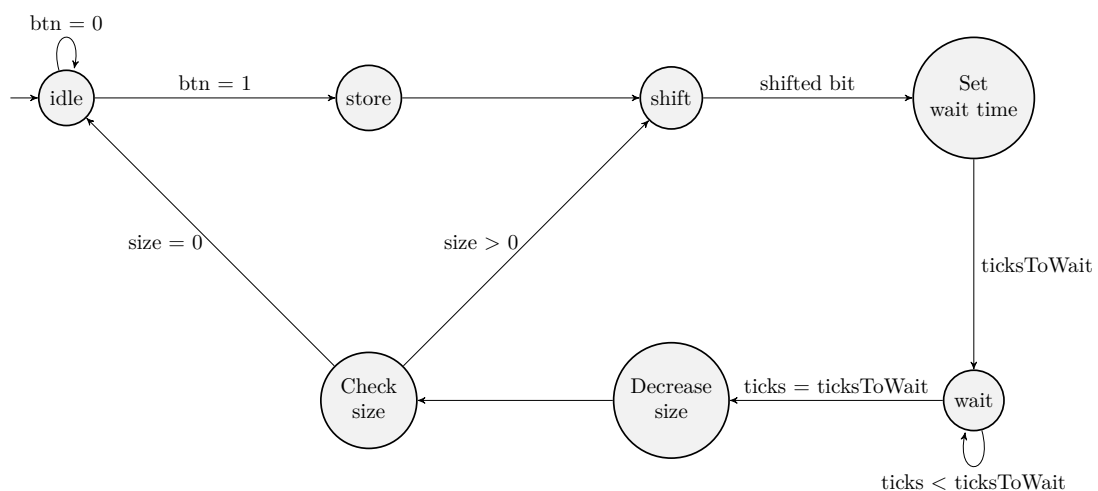

b. Details

- **Idle:** In this state, the circuit waits for user pressing the button.
- **Store:** The circuit will store morse code and morse length according to the SW[2:0].
- **Shift:** The circuit shift the bit array to the right.
- **Set wait time:**
 - + If shifted `bit` = 0 (dot), set wait time = 0.25s.
 - + If shifted `bit` = 1 (dash), set wait time = 1s.
- **Wait:** The circuit will count `ticks` until `ticks` = `ticksToWait`.
- **Decrease size:** Decrease size of morse length.
- **Check size:**
 - + If `size` = 0, return to idle state.
 - + If `size` > 0, return to shift state.

c. Expected waveform

